



L10 – FSM Implementation and Single Cycle

EECS 370 – Introduction to Computer Organization – Winter 2022

Austin, Biernacki, Das, Sample, Tang



Admin


- Project 2
 - 2A due *this* Thursday (2/10)
 - 2L due *next* Thursday (2/17)



Learning Objectives

- Be able to identify the components and trade-offs relevant to a finite state machine.
- Identify the course-granularity operation of the implementation for an FSM.

FSM for Vending Machine

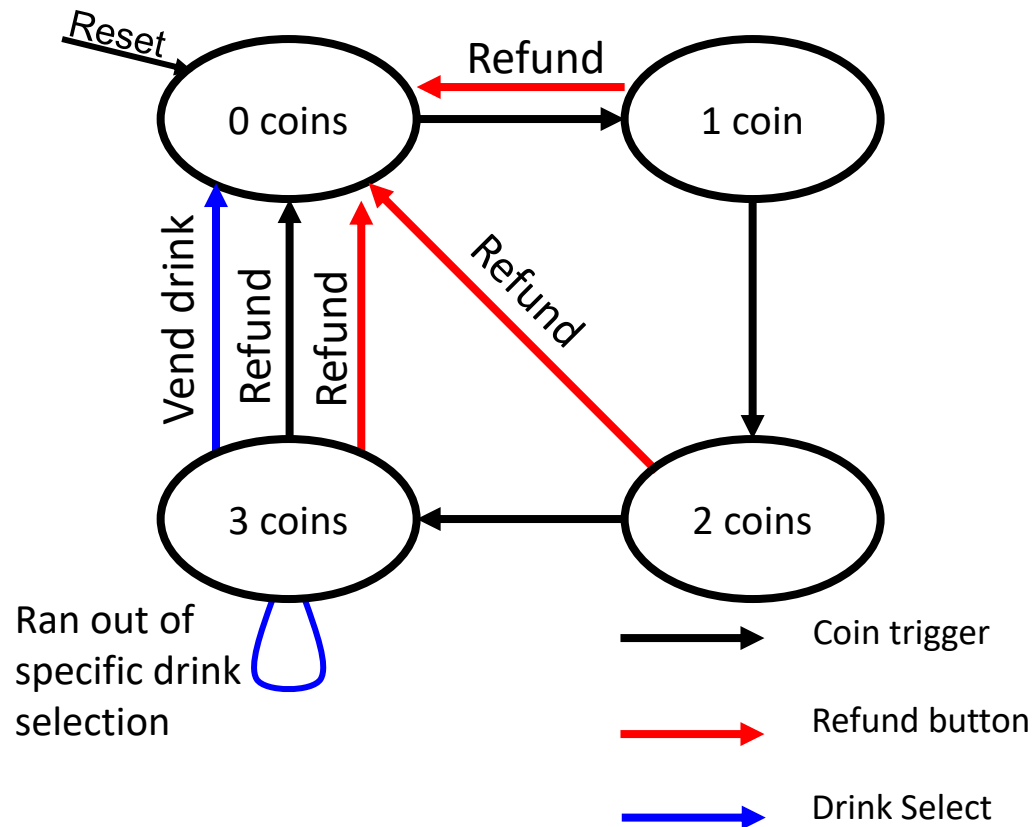


Is this a Mealy or Moore Machine?

Mealy ~ output is based on current state
AND input




Implementing a FSM

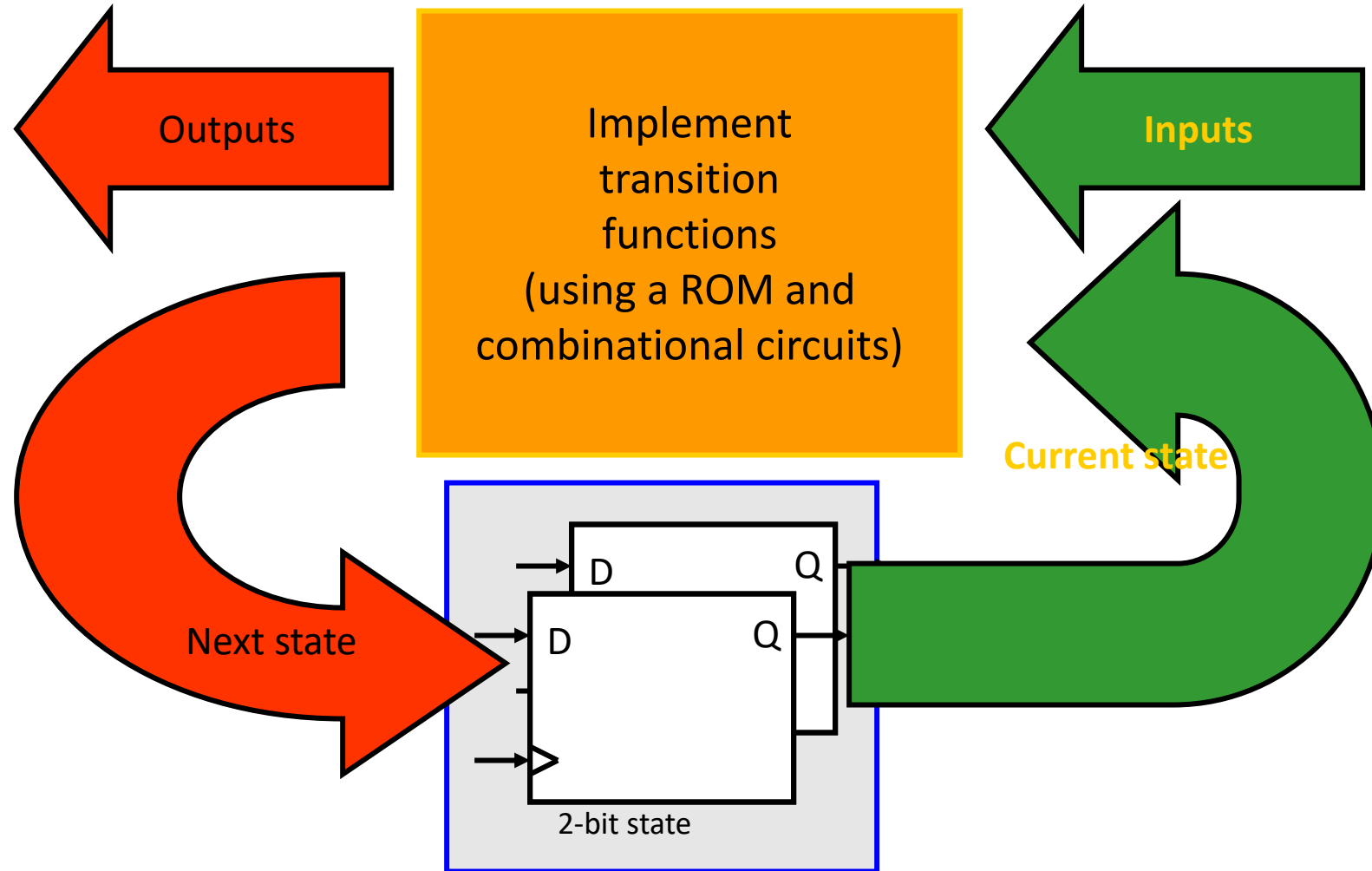


Implementing Combinational Logic (1)

 - If I have a truth table:
- I can either implement this using combinational logic:



A	B	C	O
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

 - ...or I could literally just store the entire truth table in a memory and just "address" it using the input!



Implementing Combinational Logic (2)

- Custom logic

- Pros:

- Can optimize the number of gates used

- Cons:

- Can be expensive / time consuming to make custom logic circuits

- Lookup table:

- Pros:

- Programmable ROMs (Read-Only Memories) are very cheap and can be programmed very quickly

- Cons:

- Size requirement grows exponentially with number of inputs (adding one just more bit doubles the storage requirements!)


A	B	C	O
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Add one more input...


A	B	C	D	O
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	1
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

ROMs and PROMs

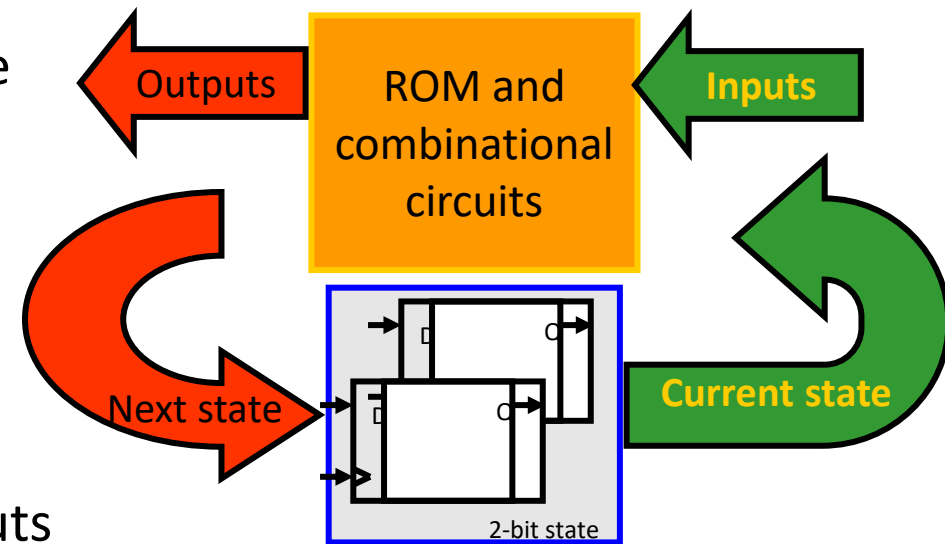- Read Only Memory
 - Array of memory values that are constant
 - Non-volatile
- Programmable Read Only Memory
 - Array of memory values that can be written exactly once (destructive writes)
- You can use ROMs to implement FSM transition functions
 - ROM inputs (i.e., ROM address): current state, primary inputs
 - ROM outputs (i.e., ROM data): next state, primary outputs



8-entry 4-bit ROM

 


ROM for Vending Machine Controller

- Use current state and inputs as address
 - 2 state bits + 22 inputs = 24 bits (address)
 - Coin, refund, 10 drink selectors, 10 sensors
- Read next state and outputs from ROM
 - 2 state bits + 11 outputs = 13 bit (memory)
 - Refund release, 10 drink latches
- We need 2^{24} entry, 13 bit ROM memories
 - 218,103,808 bits of ROM seems excessive for our cheap controller


Reducing the ROM Needed

- Idea: let's do a hybrid between combinational logic and a lookup table
 - Use basic hardware (AND / OR) gates where we can, and a ROM for everything more complicated
- Replace 10 selector inputs and 10 pressure inputs with a single bit input (drink selected)
 - Use drink selection input to specify which drink release latch to activate
 - Only allow trigger if pressure sensor indicates that there is a bottle in that selection. (10 2-bit ANDs)
- Now:
 - 2 current state bits + 3 input bits (5 bit ROM address)
 - 2 next state bits + 2 control trigger bits (4 bit memory)
 - $32 \times 4 = 128$ bit ROM (good!)

Putting It All Together

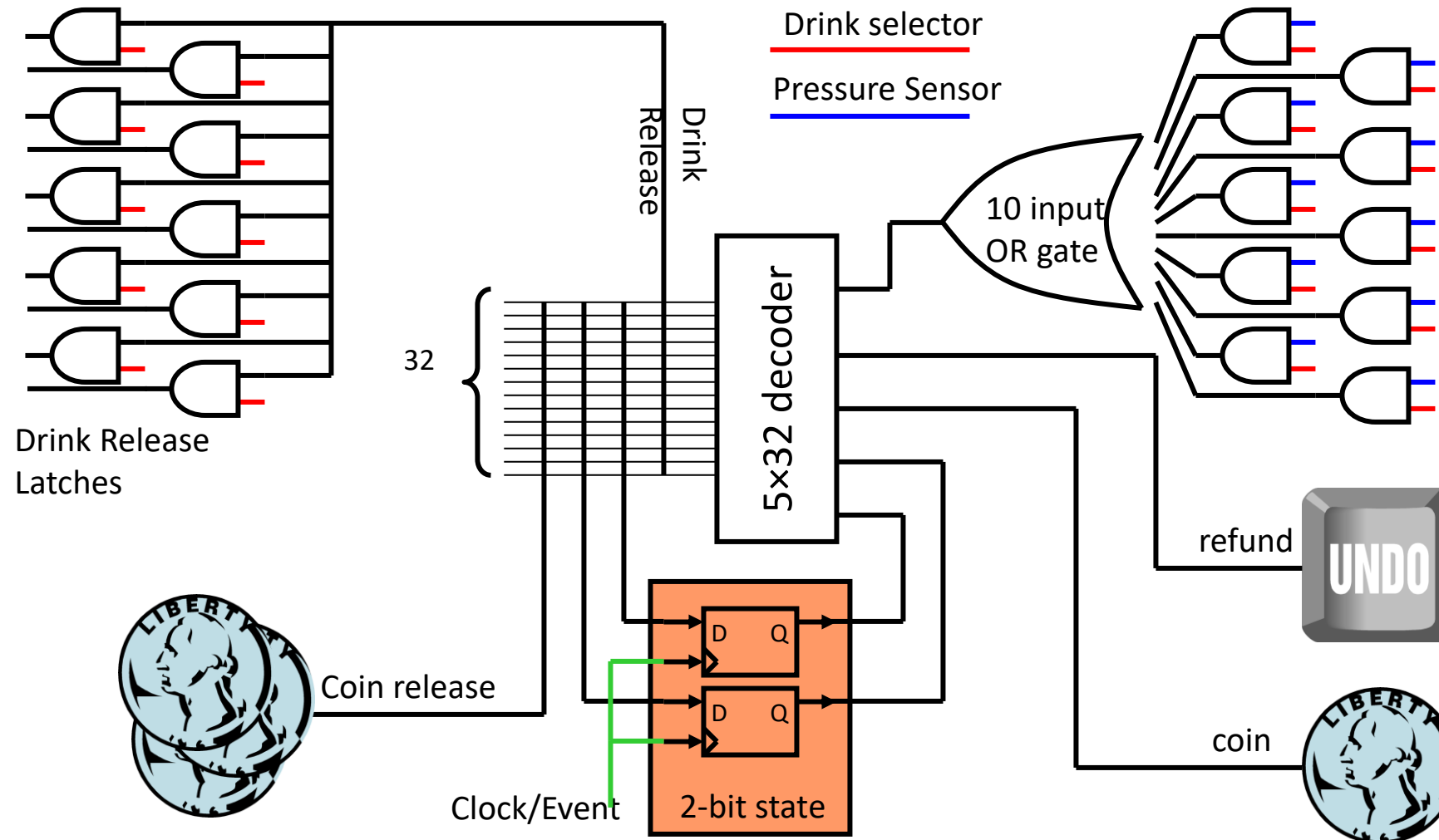

Some of the ROM Contents

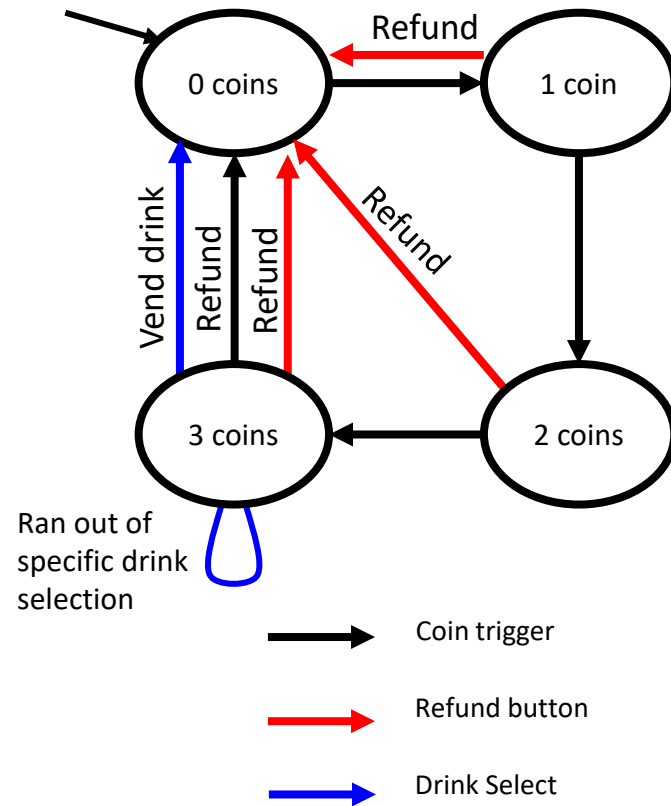

Current state	Coin trigger	Drink select	Refund button	Next state	Coin release	Drink release
0 0	0	0	0	0 0	0	0
0 0	0	0	1	0 0	0	0
0 0	0	1	0	0 0	0	0
0 0	1	0	0	0 1	0	0
0 1	1	0	0	1 0	0	0
1 0	1	0	0	1 1	0	0
1 1	0	1	0	0 0	0	1
1 1	1	0	0	0 0	1	0
... 24 more entries				... 24 more entries		


ROM address (current state, inputs)

ROM contents (next state, outputs)

Limitations of the Controller

- What happens if we make the price \$1.00?, or what if we want to accept nickels, dimes and quarters?
 - Must redesign the controller (more state, different transitions)
 - A programmable processor only needs a software upgrade.
 - If you had written software anticipating a variable price, perhaps no change is even needed
- Next Topic - Our first processor!

LC2Kx Processor as FSM

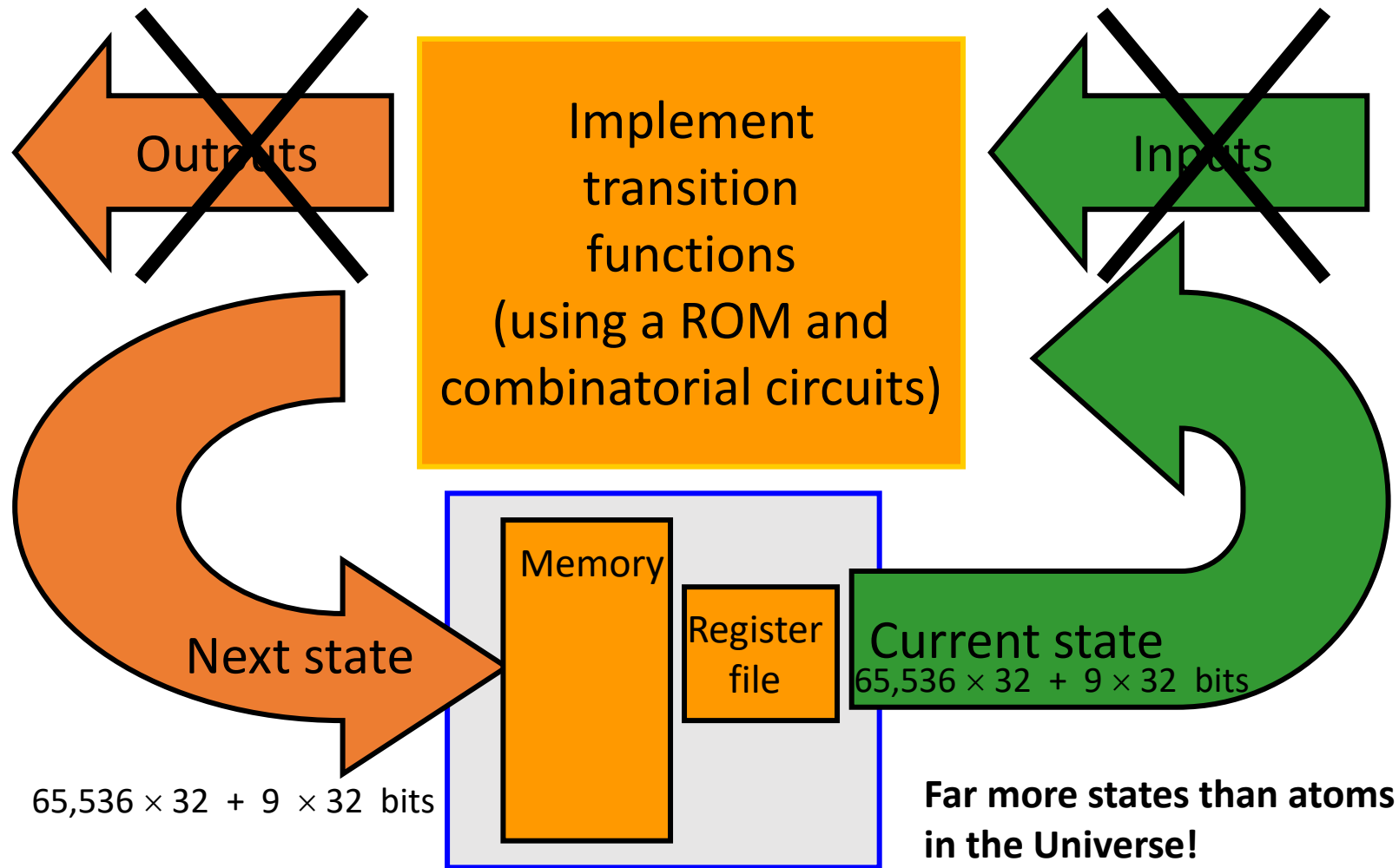



L10_2 Single-Cycle-Processor

EECS 370 – Introduction to Computer Organization – Fall 2020



Learning Objectives

- To identify the components used to implement a processor for LC-2K and understand the mapping from these components to LC-2K instructions.


Single-Cycle Processor Design

General-Purpose Processor Design


- Fetch Instructions
- Decode Instructions
 - Instructions are input to control ROM
- ROM data controls movement of data
 - Incrementing PC, reading registers, ALU control
- Clock drives it all
- Single-cycle datapath: Each instruction completes in one clock cycle

Building Blocks for the LC2K


Control

 


Compute

 

State

 


Building Blocks for the LC2K: Control

 

Connect one of the inputs to OUT based on the value of select

If (! select)
 OUT = IN1
Else
 OUT = IN2

Building Blocks for the LC2K: Control

 


Decoder activates one of the output lines based on the input

IN	OUT
<u>210</u>	<u>76543210</u>
000	00000001
001	00000010
010	00000100
011	00001000
etc.	

ROM stores preset data in each location.
Give address to access data.

Building Blocks for the LC2K: Compute

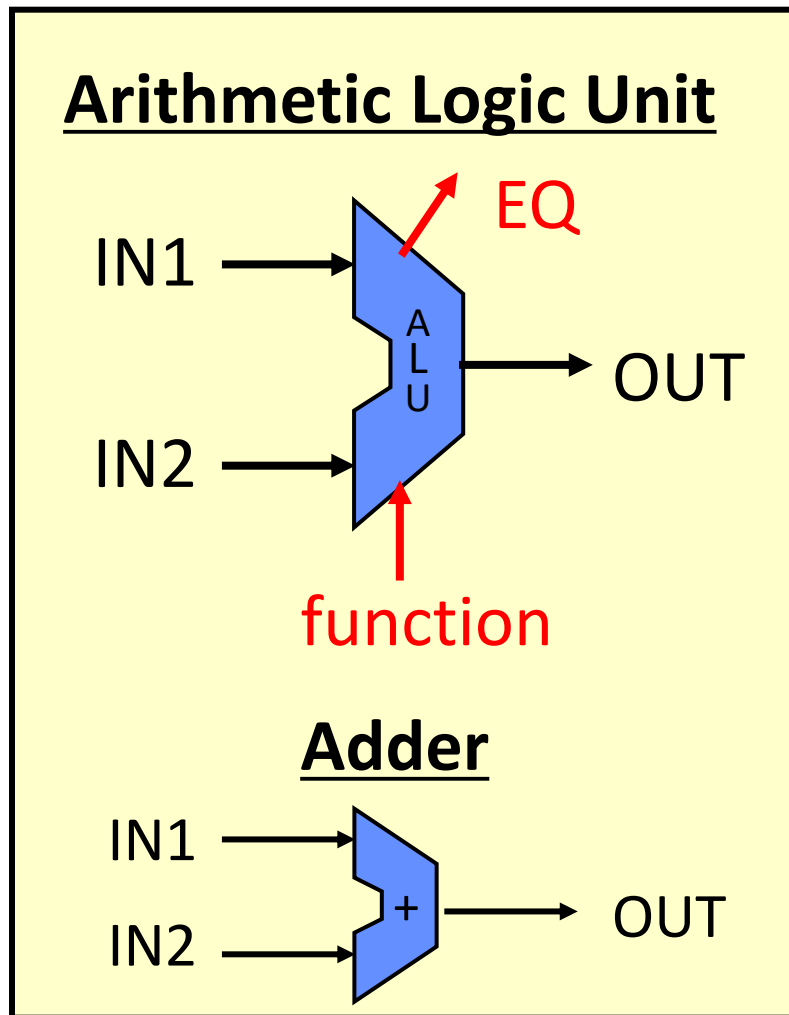

Perform basic arithmetic functions

$$\text{OUT} = f(\text{IN1}, \text{IN2})$$

$$\text{EQ} = (\text{IN1} == \text{IN2})$$

For LC2K:

$f=0$ is add


$f=1$ is nor

For other processors, there are many more functions.

Just adds

Building Blocks for the LC2K: Compute

Sign Extension Unit

 

Sign extend input by replicating the MSB to width of output


$$\text{OUT}(31:0) = \text{SE}(\text{IN}(15:0))$$

$$\text{OUT}(31:16) = \text{IN}(15)$$

$$\text{OUT}(15:0) = \text{IN}(15:0)$$

Useful when compute unit is wider than data

Building Blocks for the LC2K: State

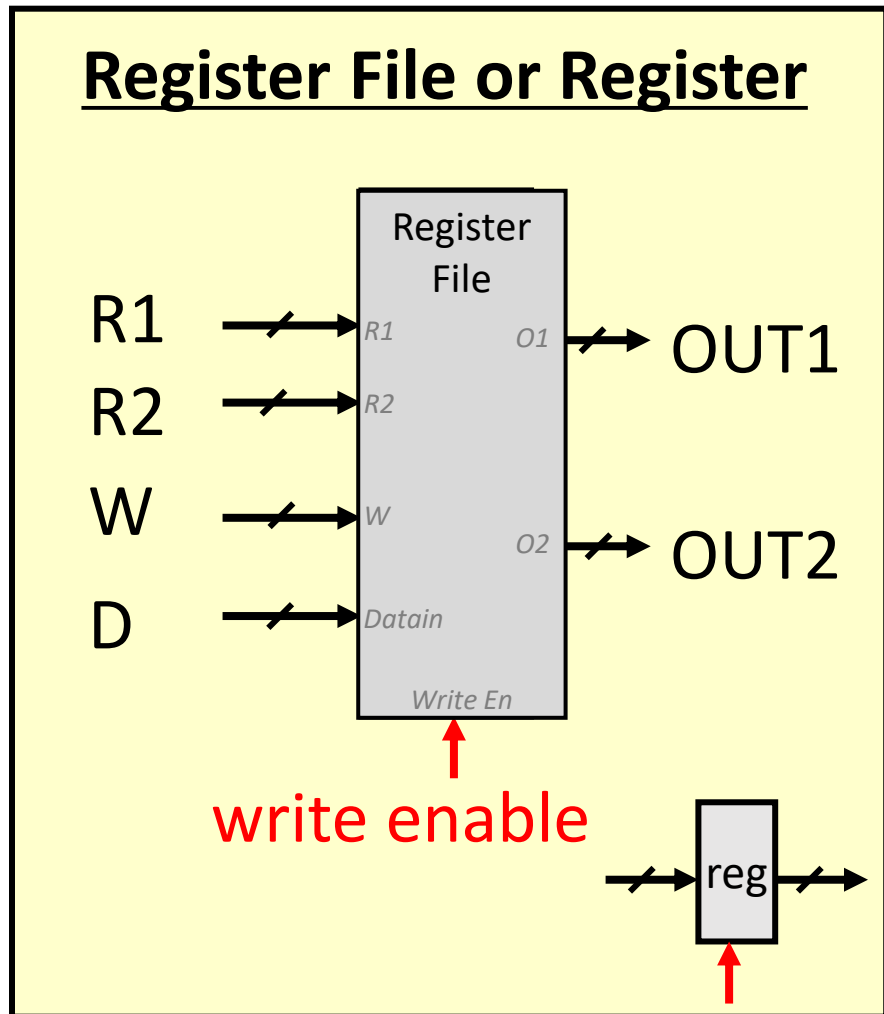

Small/fast memory to store temporary values


n entries (LC2 = 8)

r read ports (LC2 = 2)

w write ports (LC2 = 1)

- * R_i specifies register number to read
- * W specifies register number to write
- * D specifies data to write

Building Blocks for the LC2K: State

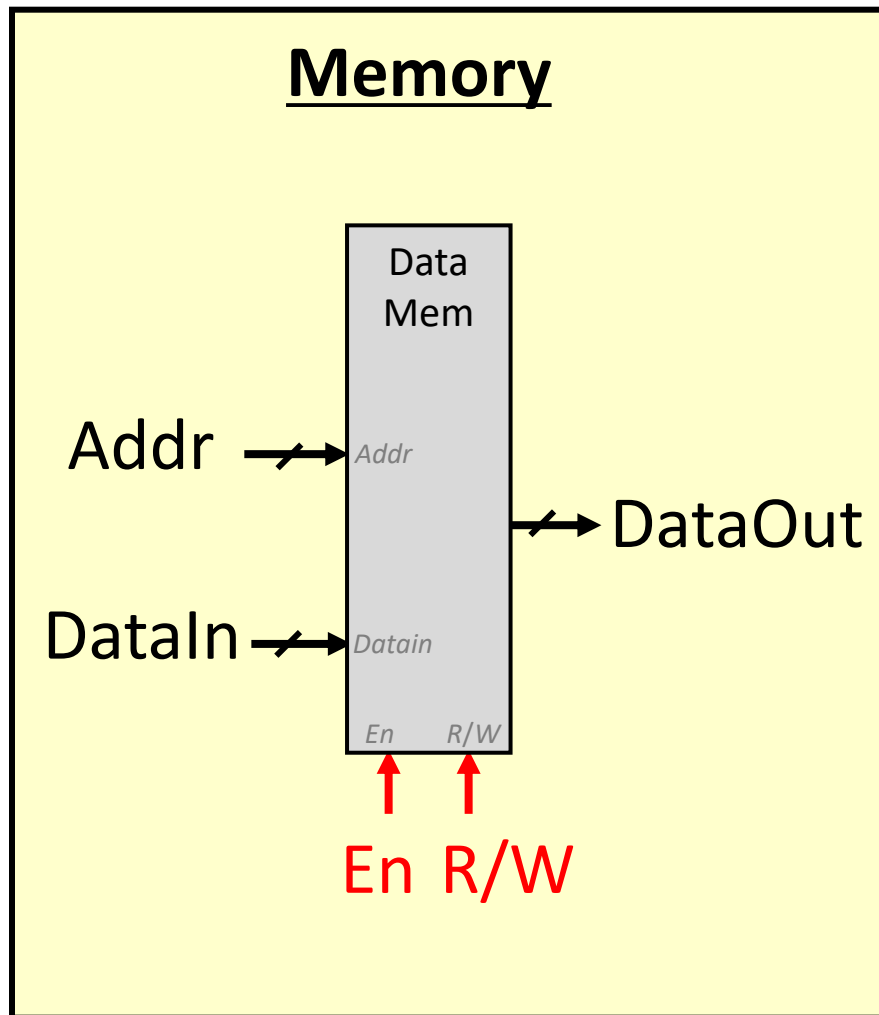


Slower storage structure to hold large amounts of stuff.

Use 2 memories for LC2


- * Instructions
- * Data
- * 65,536 total words

Review: LC2K Instruction Formats

 - Tells you which bit positions mean what
- R-type instructions (opcodes add 000, nor 001)



 - I-type instructions (opcodes lw 010, sw 011, beq 100)





L10_3 LC2K-Datapath

EECS 370 – Introduction to Computer Organization – Fall 2020




Single-Cycle Processor Design


General-Purpose Processor Design


- Fetch Instructions
- Decode Instructions
 - Instructions are input to control ROM
- ROM data controls movement of data
 - Incrementing PC, reading registers, ALU control
- Clock drives it all


Single-cycle datapath:

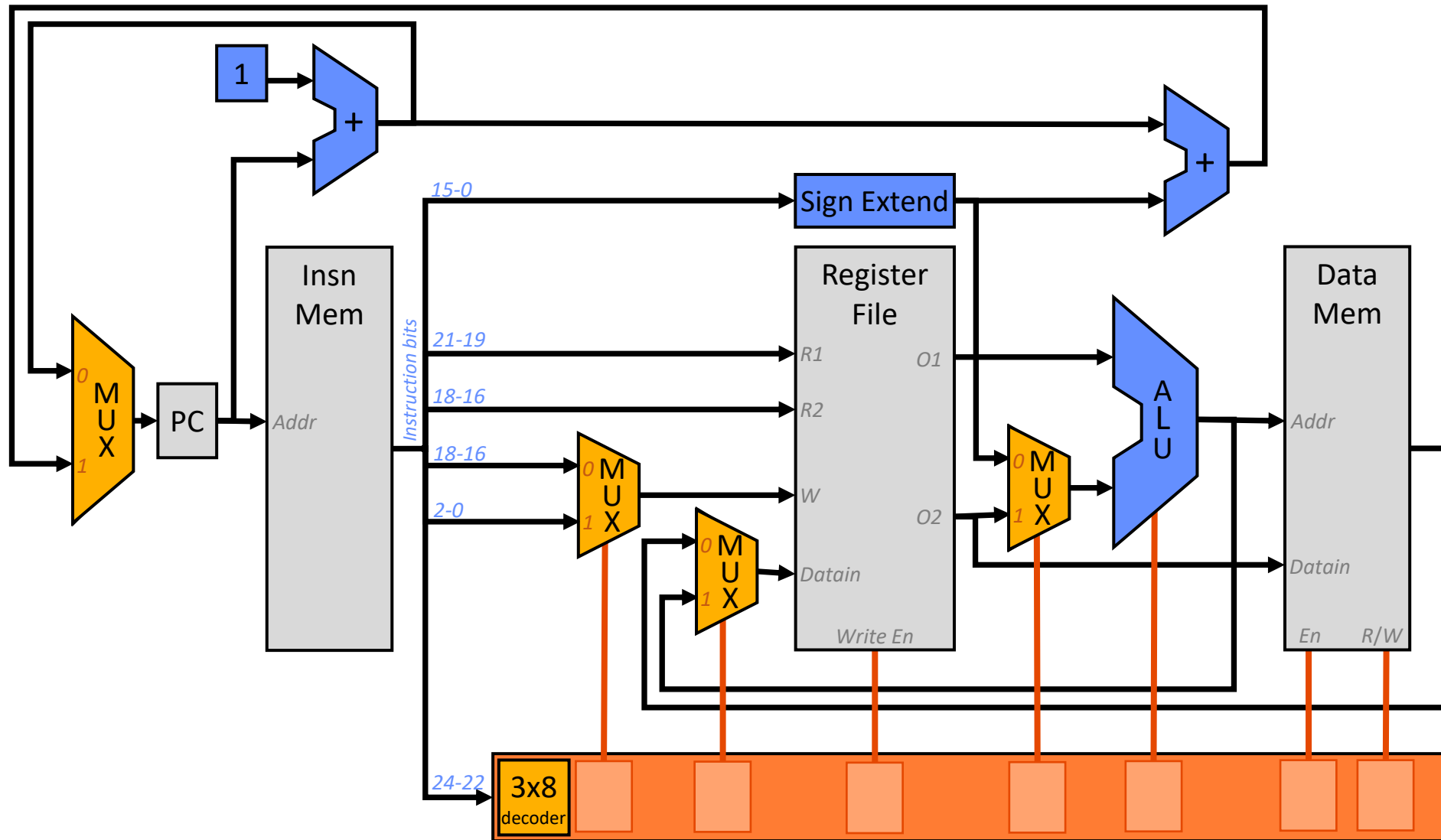
Each instruction completes in one clock cycle




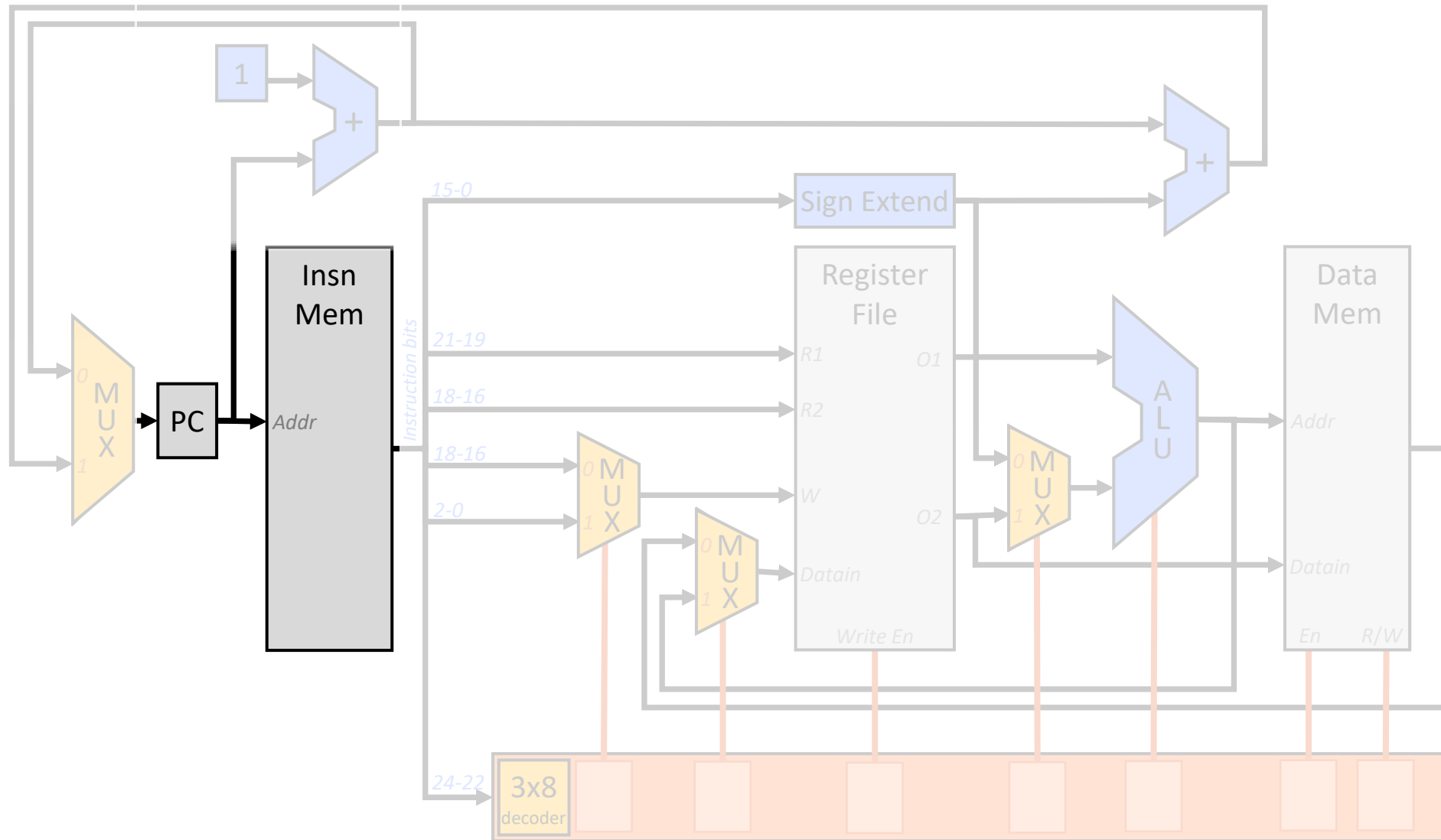

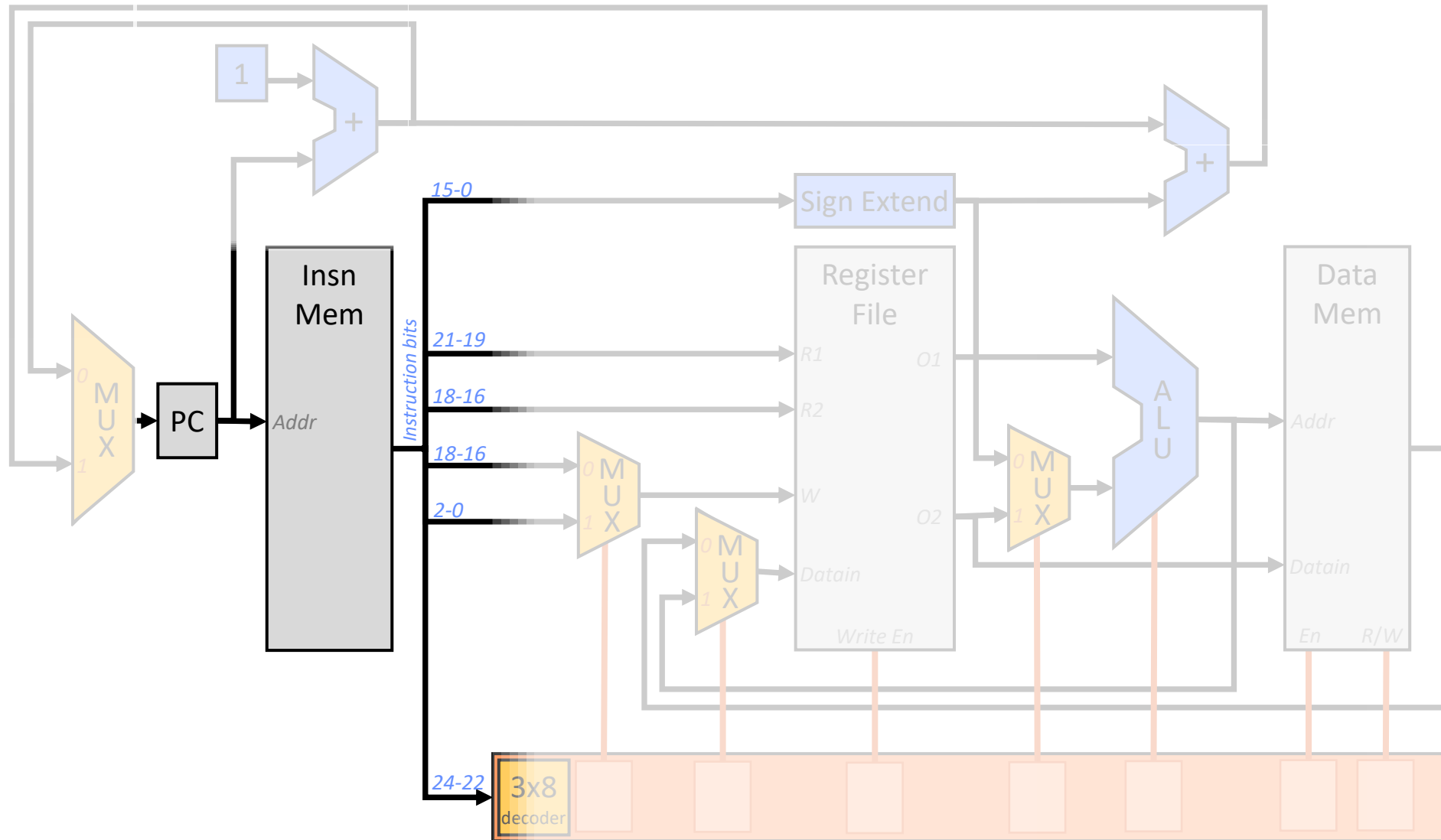

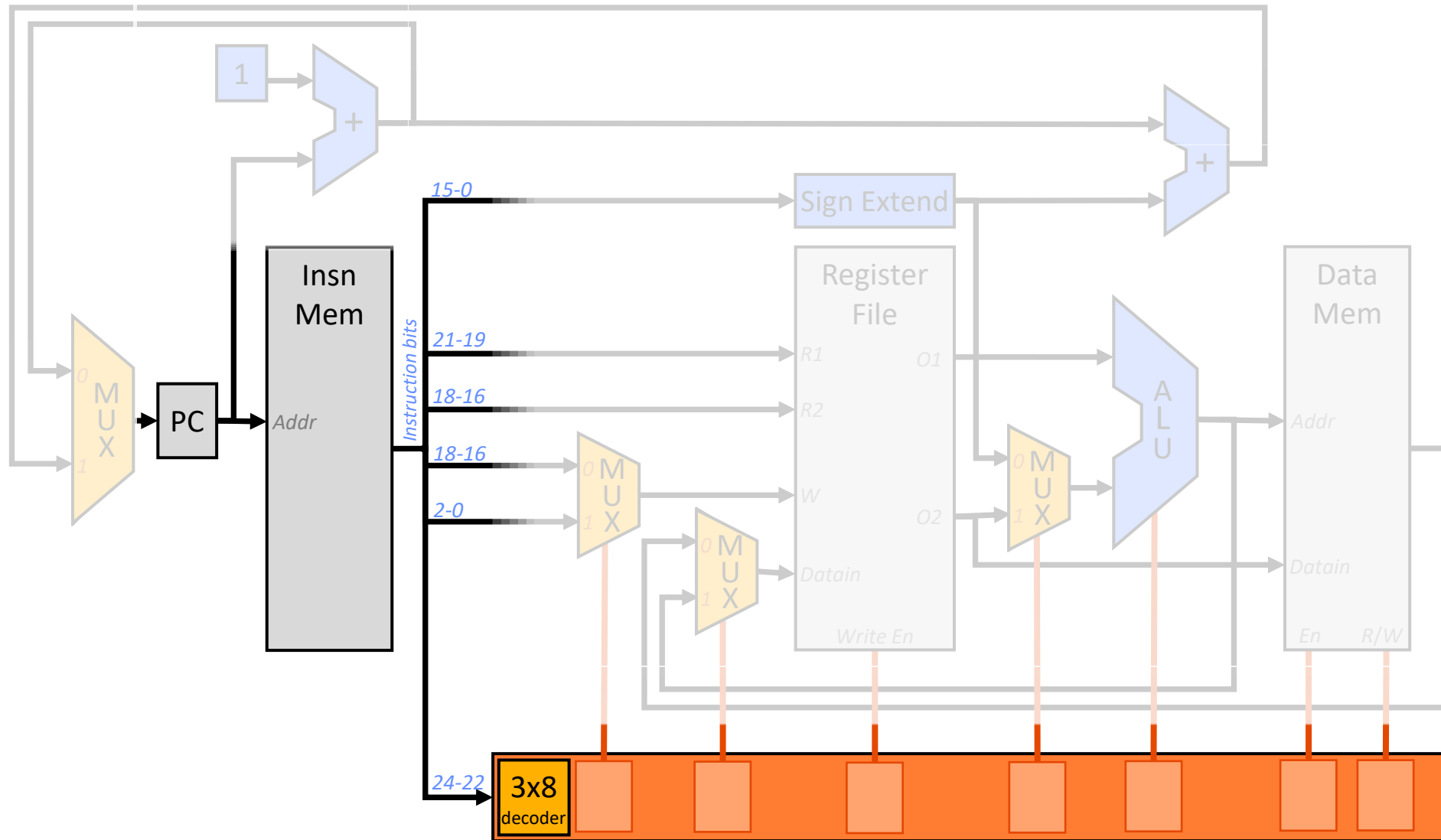


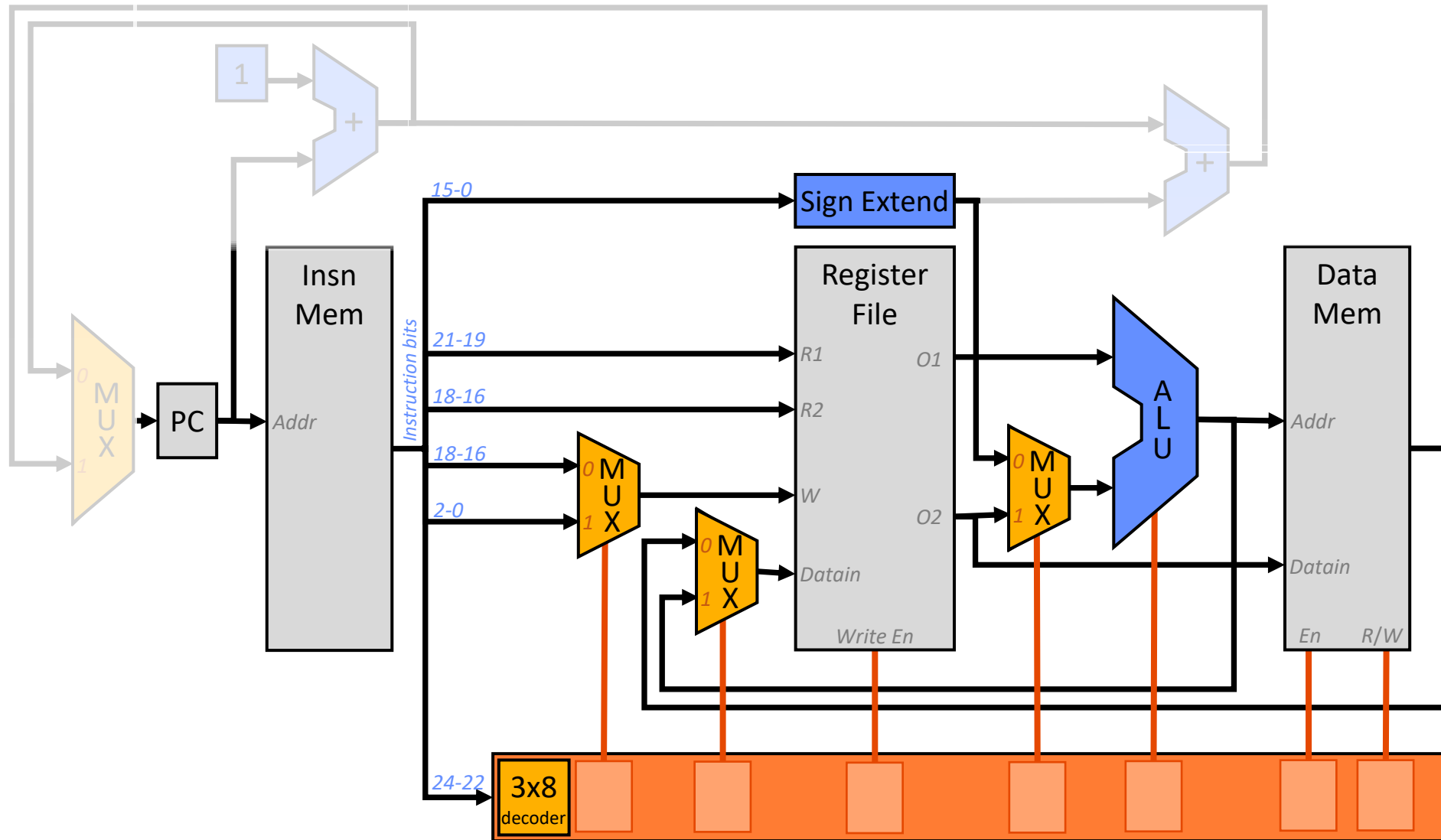

 


ADD	Instruction	add regA, regB, destR					
	Functionality	destR = regA + regB; PC = PC+1					
	R-Type	31-25	24-22	21-19	18-16	15-3	2-0
		opcode	regA	regB			destR

LC2K Single-Cycle Processor

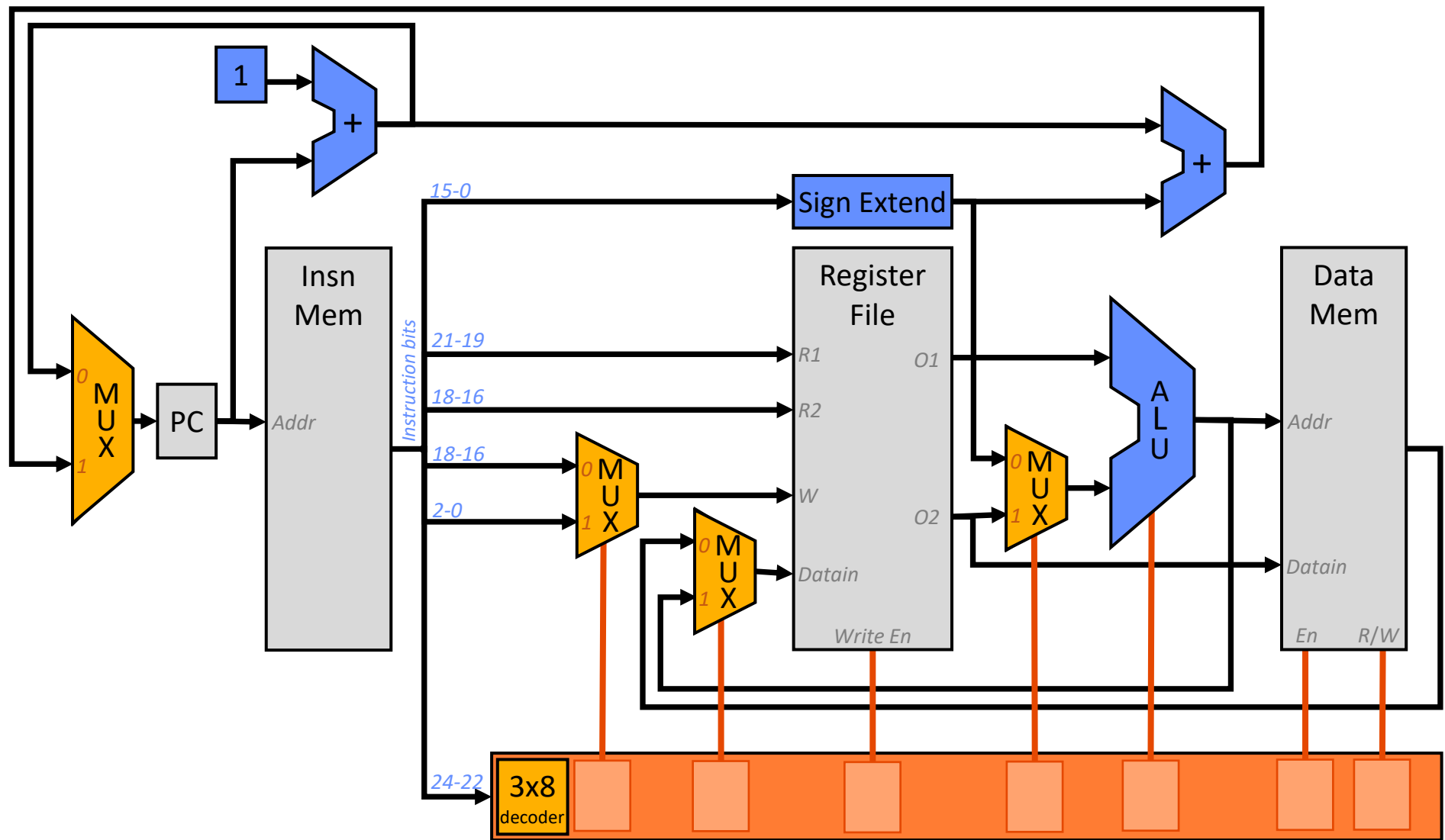


ADD	Instruction	add regA, regB, destR					
	Functionality	destR = regA + regB; PC = PC+1					
	R-Type	31-25	24-22	21-19	18-16	15-3	2-0
		opcode	regA	regB			destR

LC2K Single-Cycle Processor

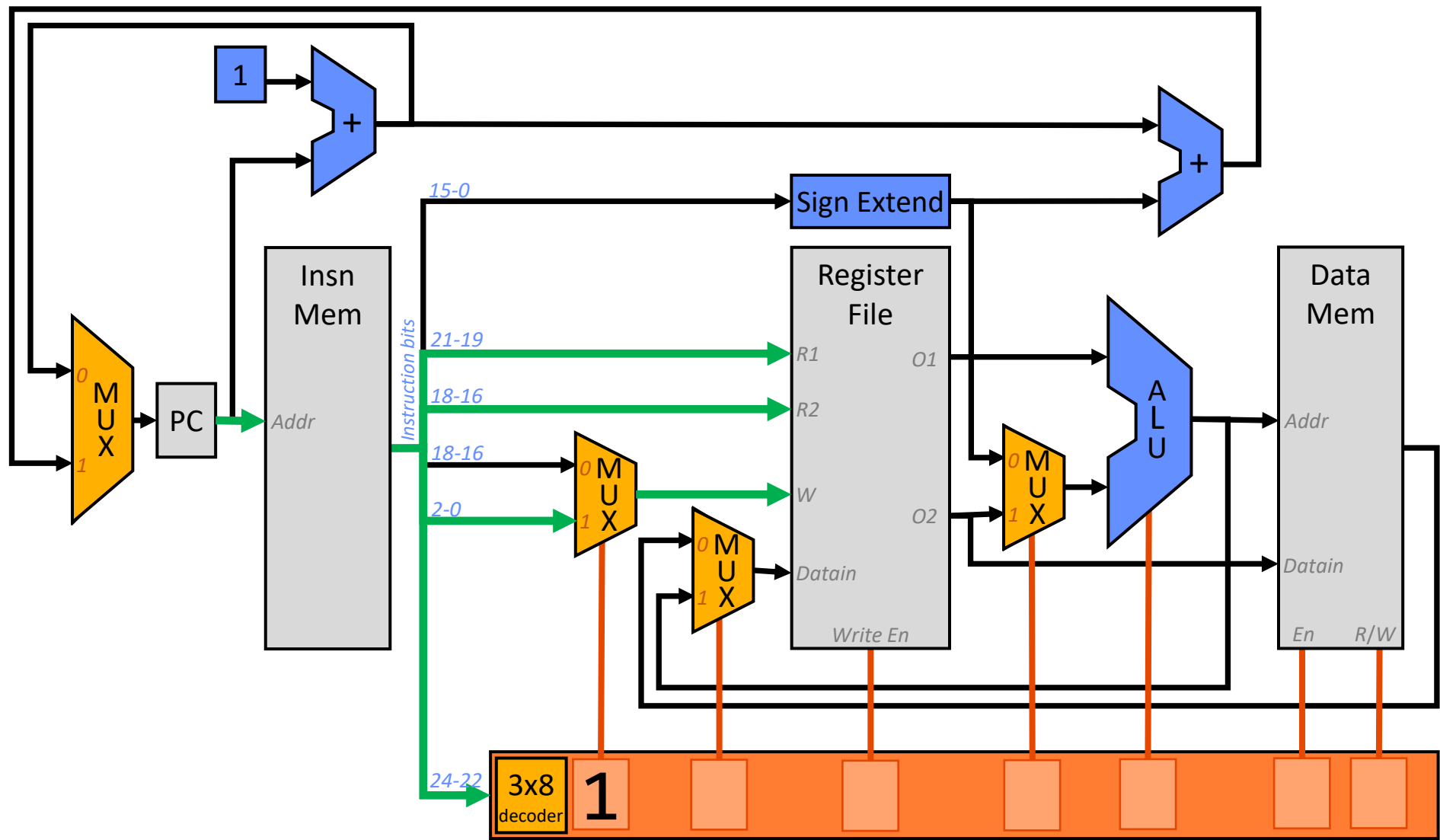


ADD	Instruction	add regA, regB, destR					
	Functionality	destR = regA + regB; PC = PC+1					
	R-Type	31-25	24-22	21-19	18-16	15-3	2-0
		opcode	regA	regB			destR

LC2K Single-Cycle Processor

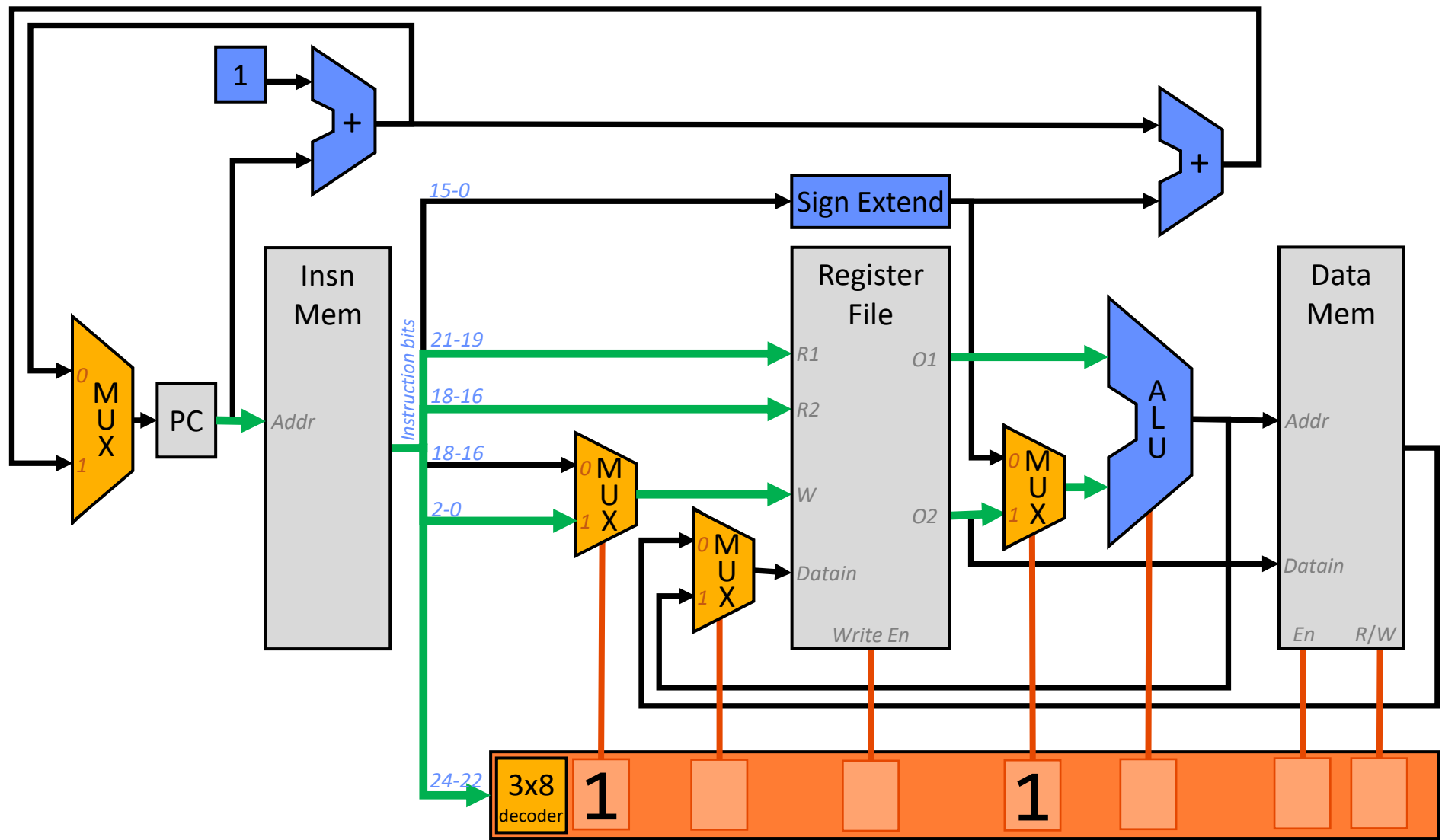


ADD	Instruction	add regA, regB, destR					
	Functionality	destR = regA + regB; PC = PC+1					
	R-Type	31-25	24-22	21-19	18-16	15-3	2-0
		opcode	regA	regB			destR

LC2K Single-Cycle Processor

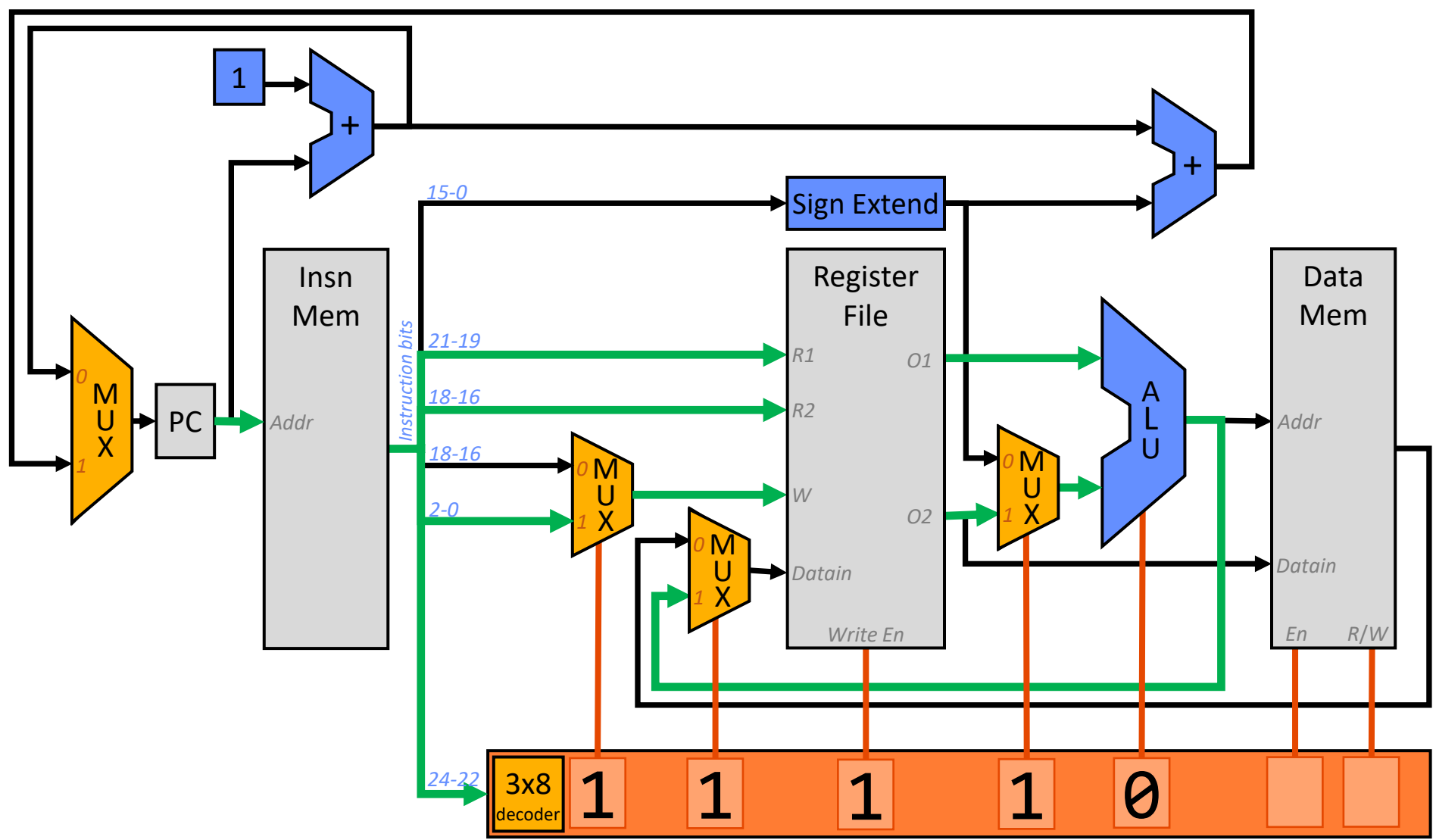


ADD	Instruction	add regA, regB, destR					
	Functionality	destR = regA + regB; PC = PC+1					
	R-Type	31-25	24-22	21-19	18-16	15-3	2-0
		opcode	regA	regB			destR

LC2K Single-Cycle Processor

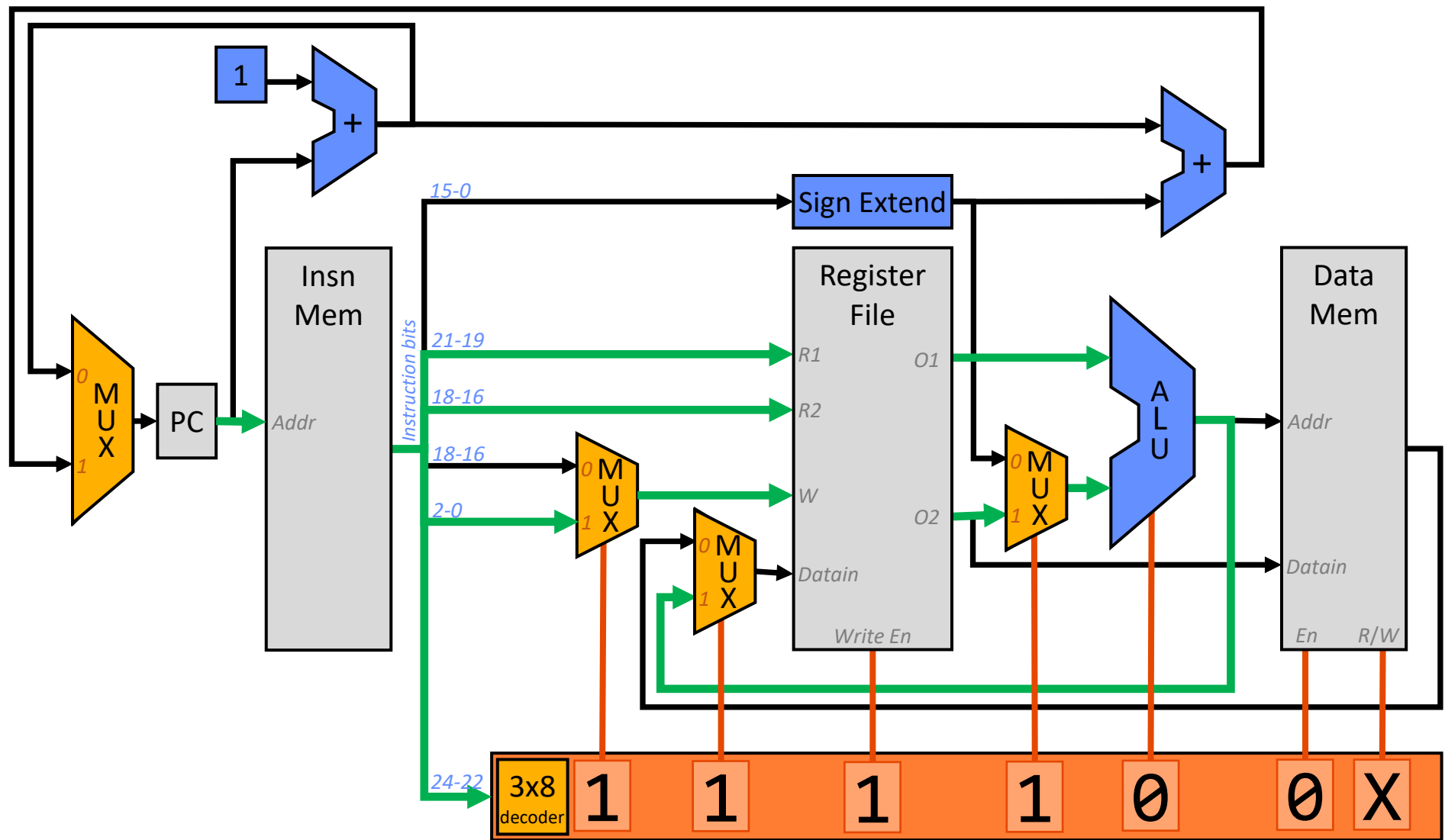


ADD	Instruction	add regA, regB, destR					
	Functionality	destR = regA + regB; PC = PC+1					
	R-Type	31-25	24-22	21-19	18-16	15-3	2-0
		opcode	regA	regB			destR

LC2K Single-Cycle Processor

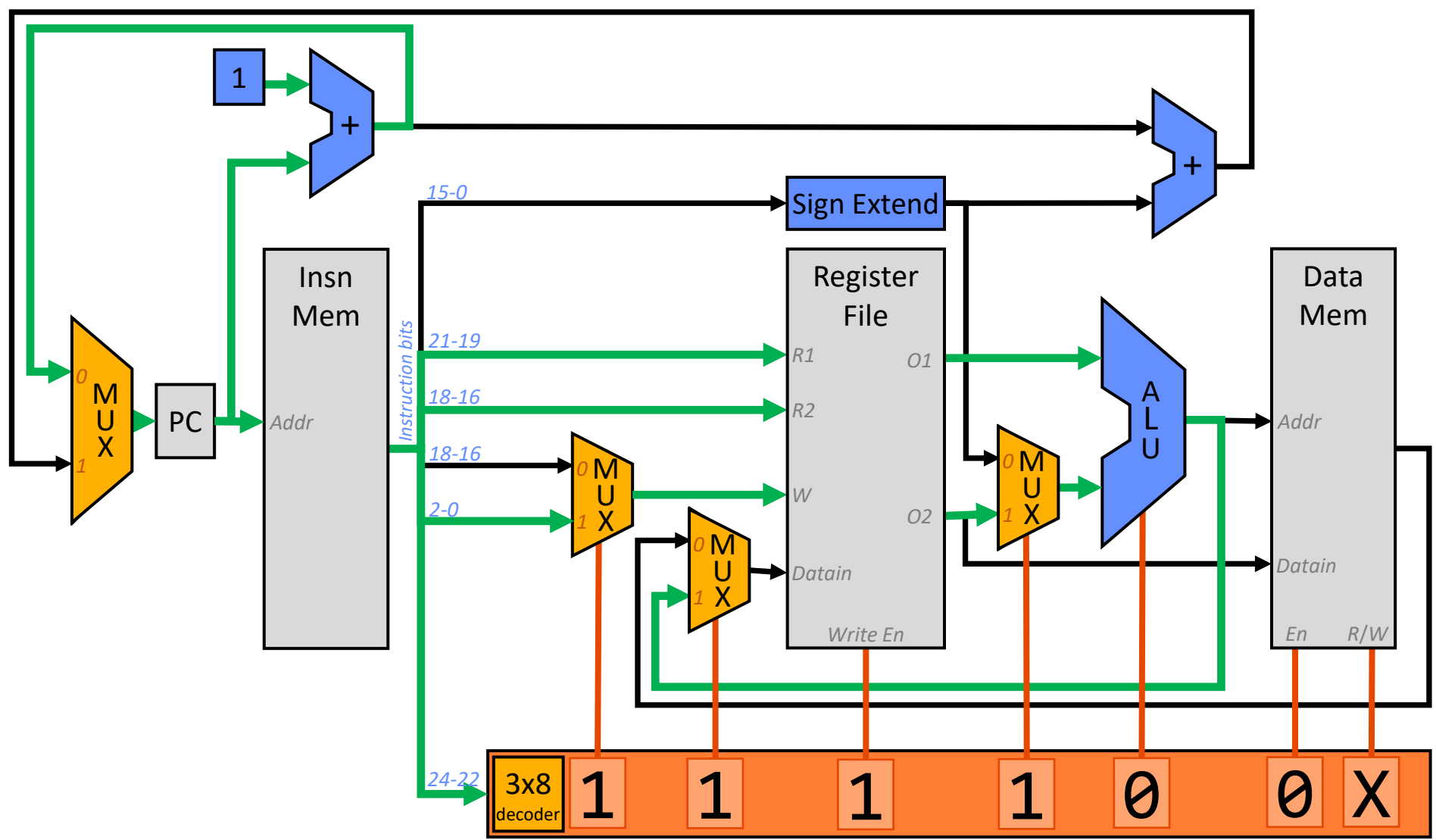

NOR	Instruction	nor regA, regB, destR					
	Functionality	destR = ~(regA regB); PC = PC+1					
	R-Type	31-25	24-22	21-19	18-16	15-3	2-0
		opcode	regA	regB			destR


LC2K Single-Cycle Processor

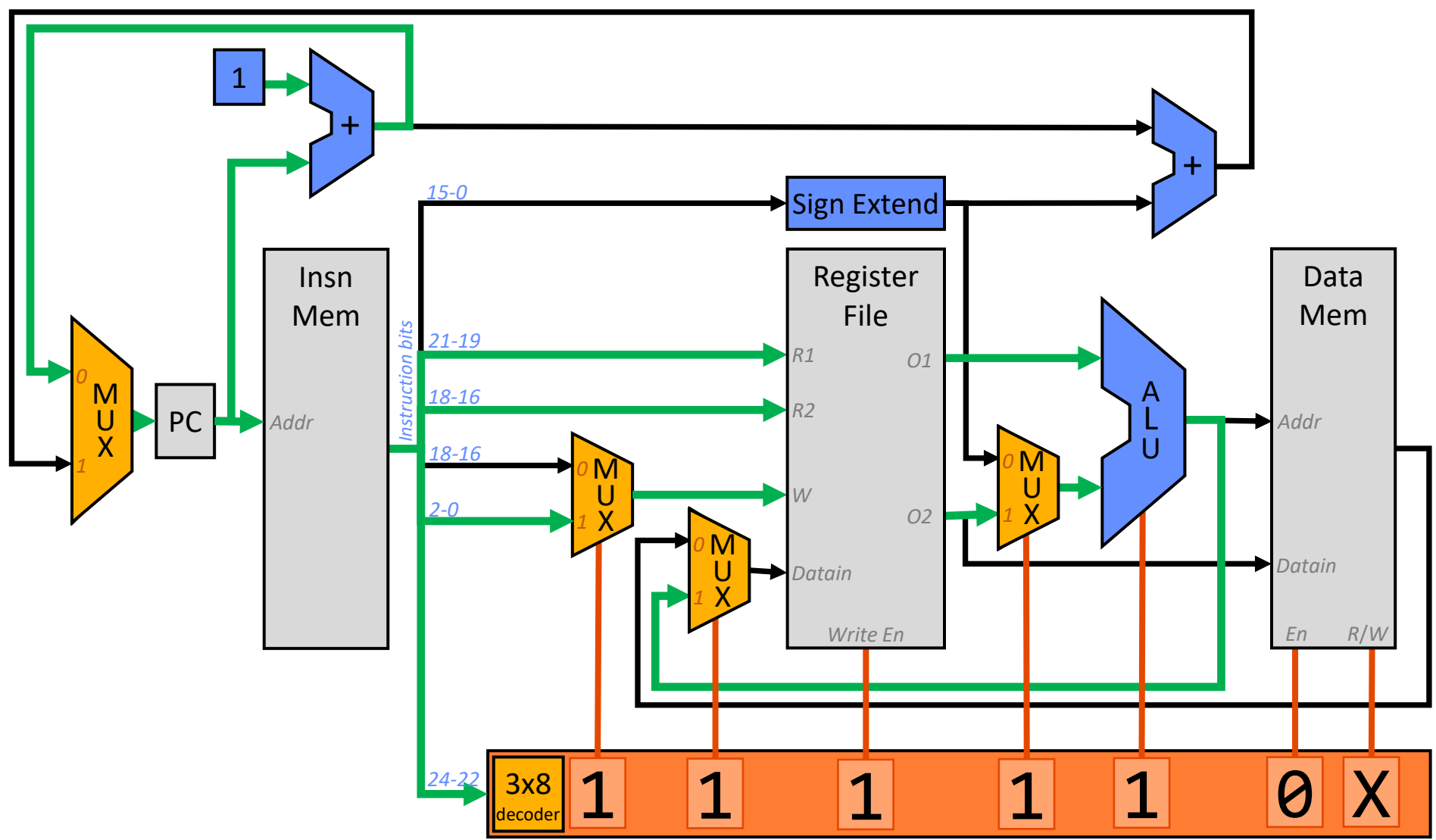

LW

Instruction	lw regA, regB, offset				
Functionality	regB = M[regA + offset]; PC = PC+1				
I-Type	31-25	24-22	21-19	18-16	15-0
	opcode	regA	regB	destR	


LC2K Single-Cycle Processor

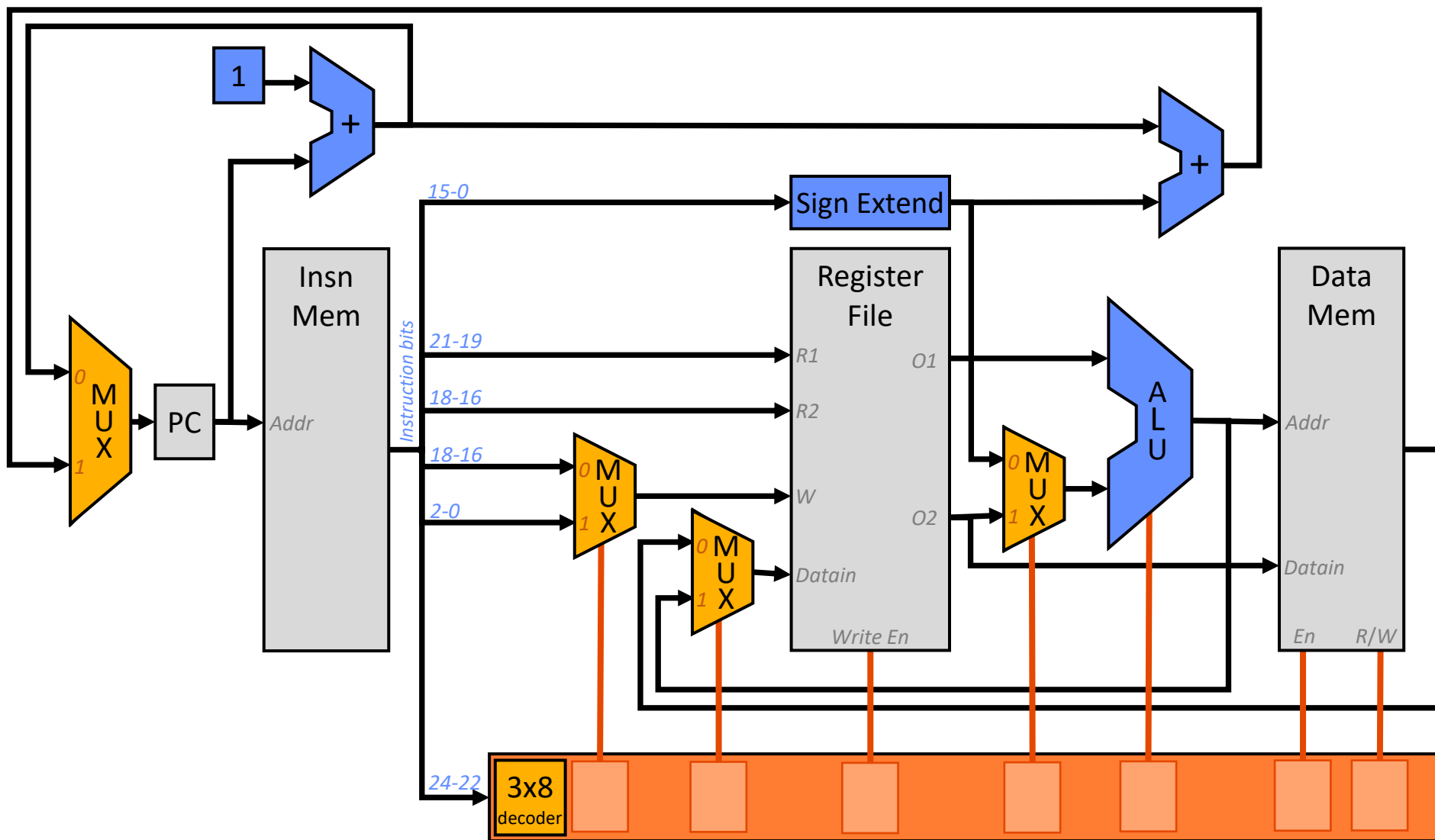

LW

Instruction	lw regA, regB, offset				
Functionality	regB = M[regA + offset]; PC = PC+1				
I-Type	31-25	24-22	21-19	18-16	15-0
	opcode	regA	regB	destR	


LC2K Single-Cycle Processor

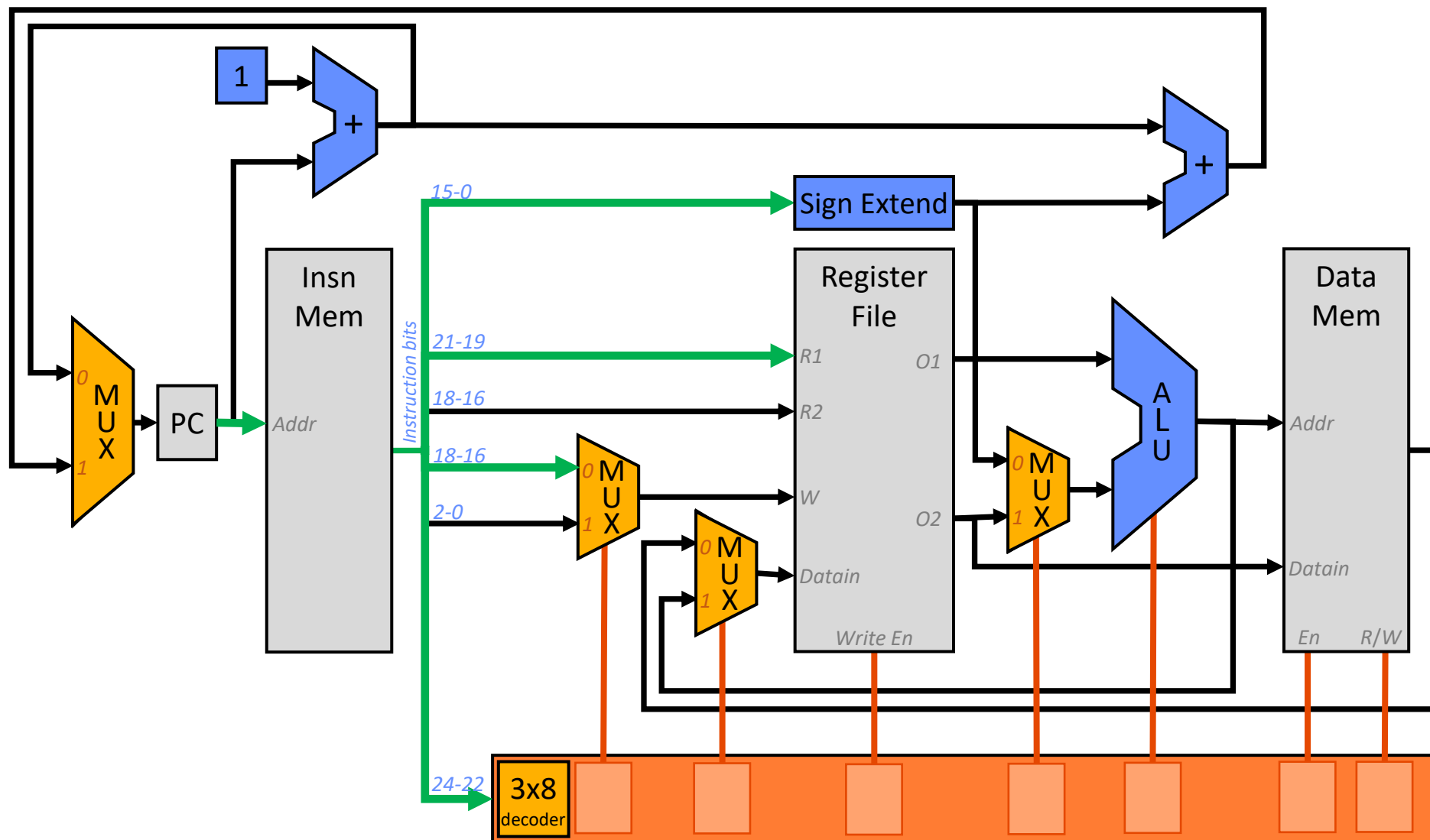

LW

Instruction	lw regA, regB, offset				
Functionality	regB = M[regA + offset]; PC = PC+1				
I-Type	31-25	24-22	21-19	18-16	15-0
	opcode	regA	regB	destR	


LC2K Single-Cycle Processor

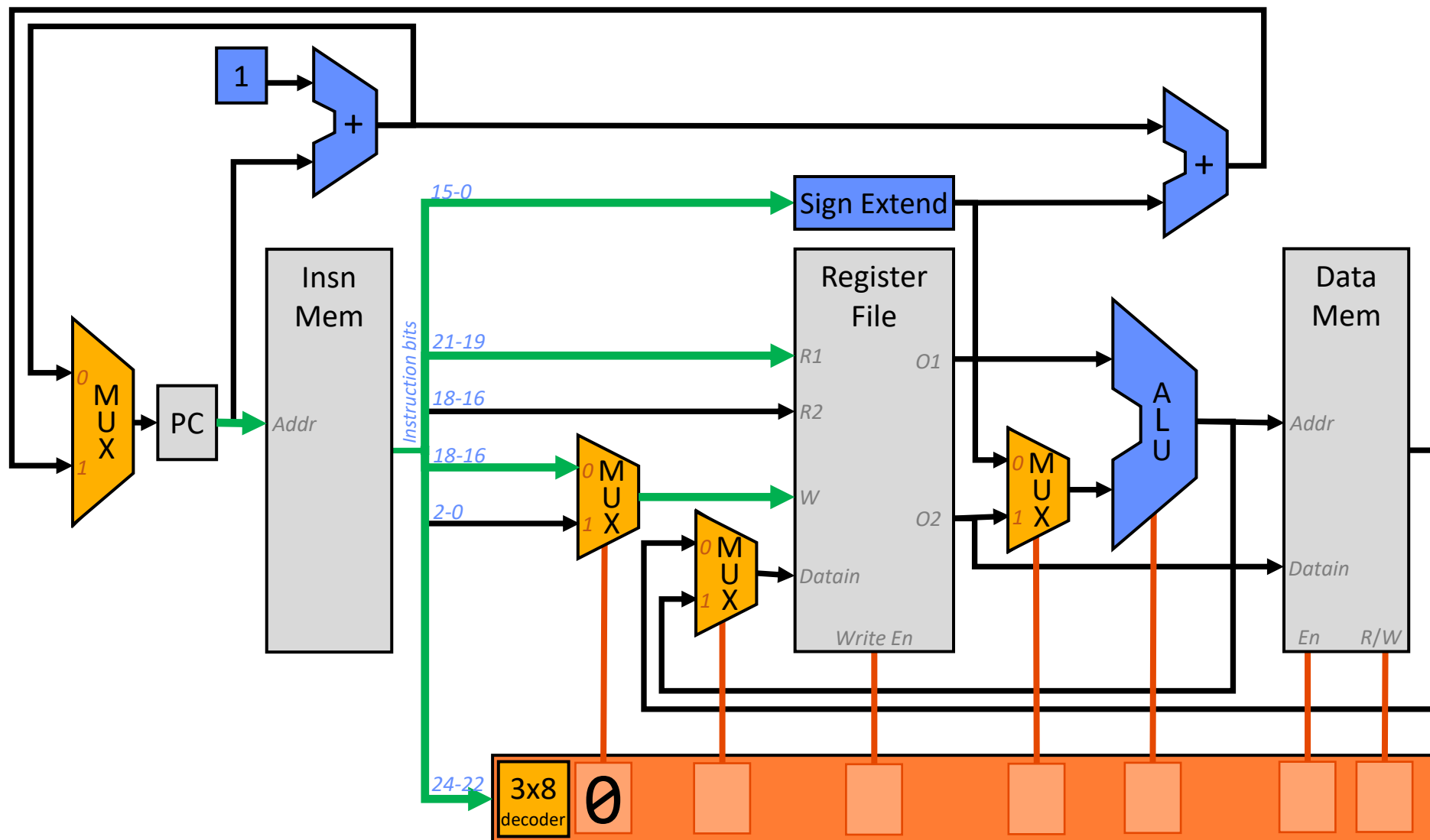

LW

Instruction	lw regA, regB, offset				
Functionality	regB = M[regA + offset]; PC = PC+1				
I-Type	31-25	24-22	21-19	18-16	15-0
	opcode	regA	regB	destR	


LC2K Single-Cycle Processor

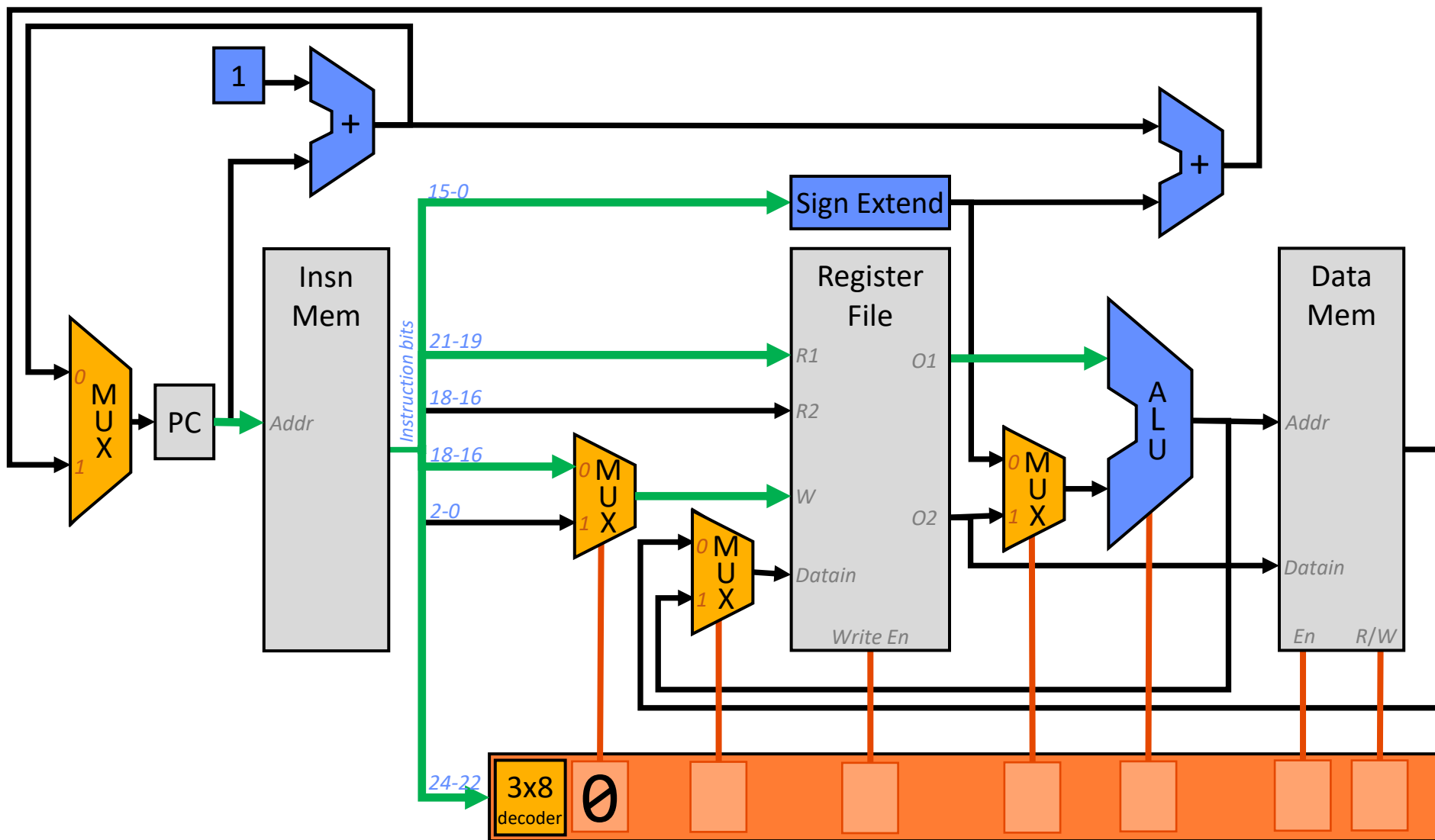

LW

Instruction	lw regA, regB, offset				
Functionality	regB = M[regA + offset]; PC = PC+1				
I-Type	31-25	24-22	21-19	18-16	15-0
	opcode	regA	regB	destR	


LC2K Single-Cycle Processor

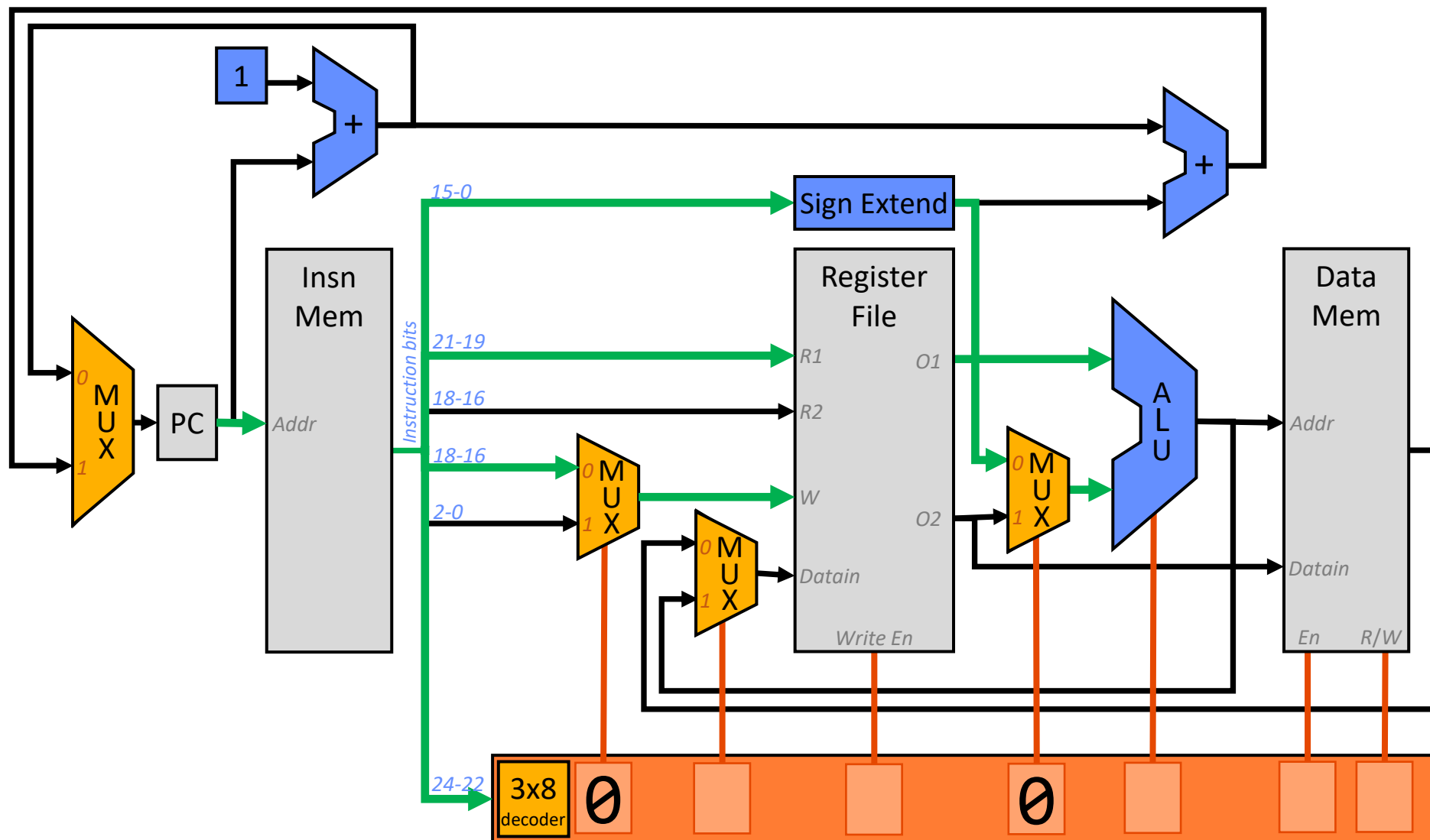

LW

Instruction	lw regA, regB, offset				
Functionality	regB = M[regA + offset]; PC = PC+1				
I-Type	31-25	24-22	21-19	18-16	15-0
	opcode	regA	regB	destR	


LC2K Single-Cycle Processor

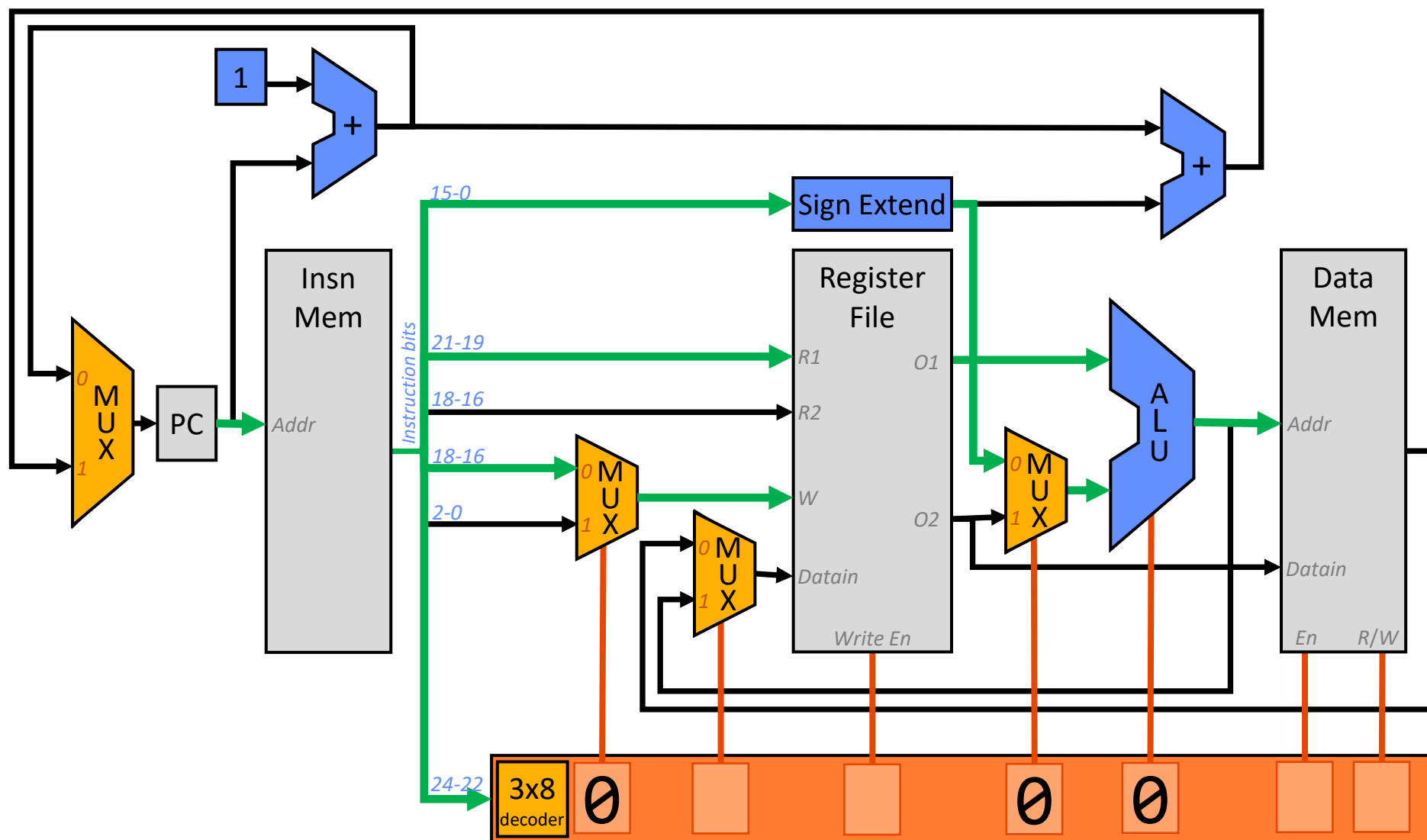

LW

Instruction	lw regA, regB, offset				
Functionality	regB = M[regA + offset]; PC = PC+1				
I-Type	31-25	24-22	21-19	18-16	15-0
	opcode	regA	regB	destR	


LC2K Single-Cycle Processor

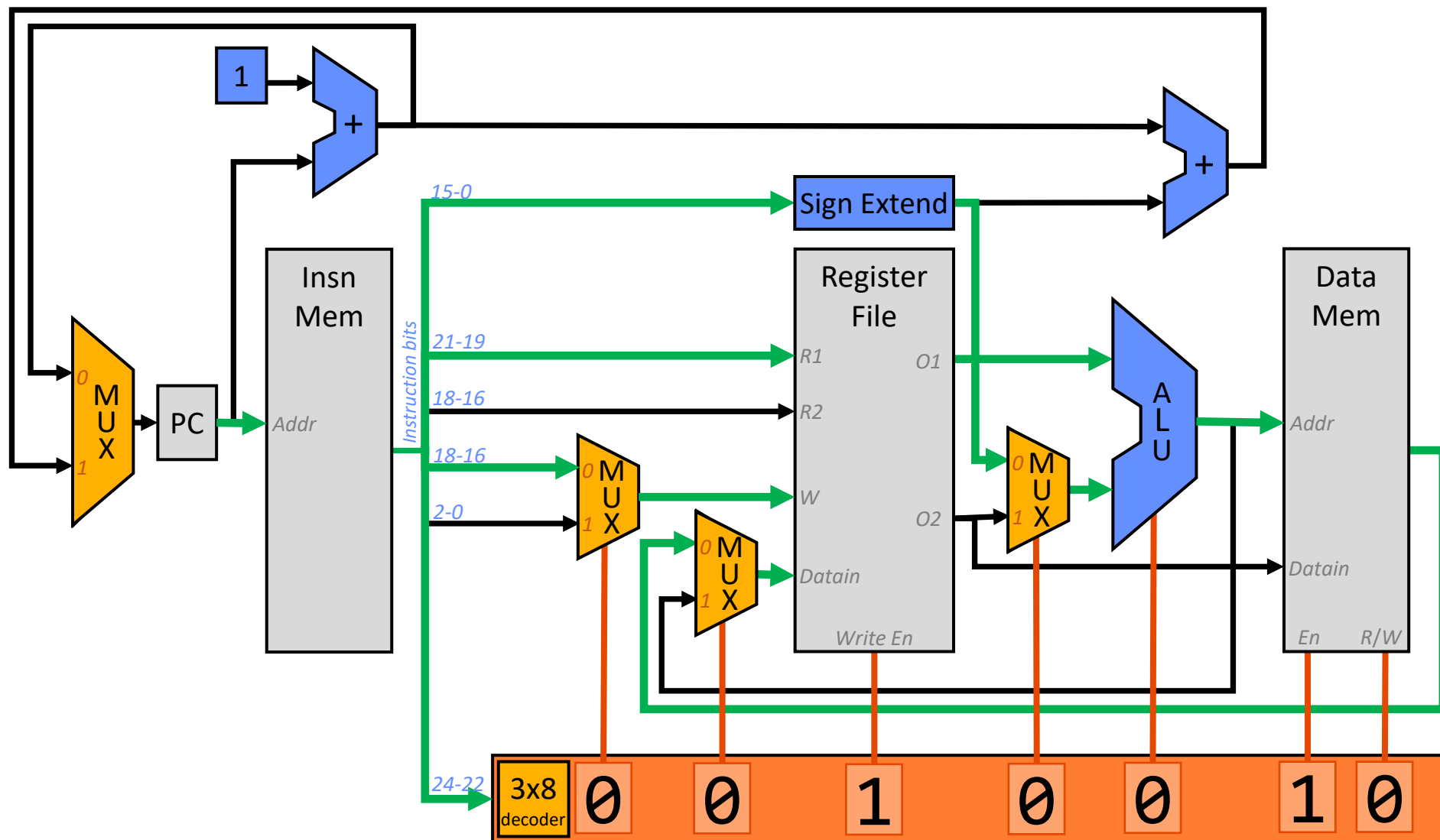

LW

Instruction	lw regA, regB, offset				
Functionality	regB = M[regA + offset]; PC = PC+1				
I-Type	31-25	24-22	21-19	18-16	15-0
	opcode	regA	regB	destR	


LC2K Single-Cycle Processor

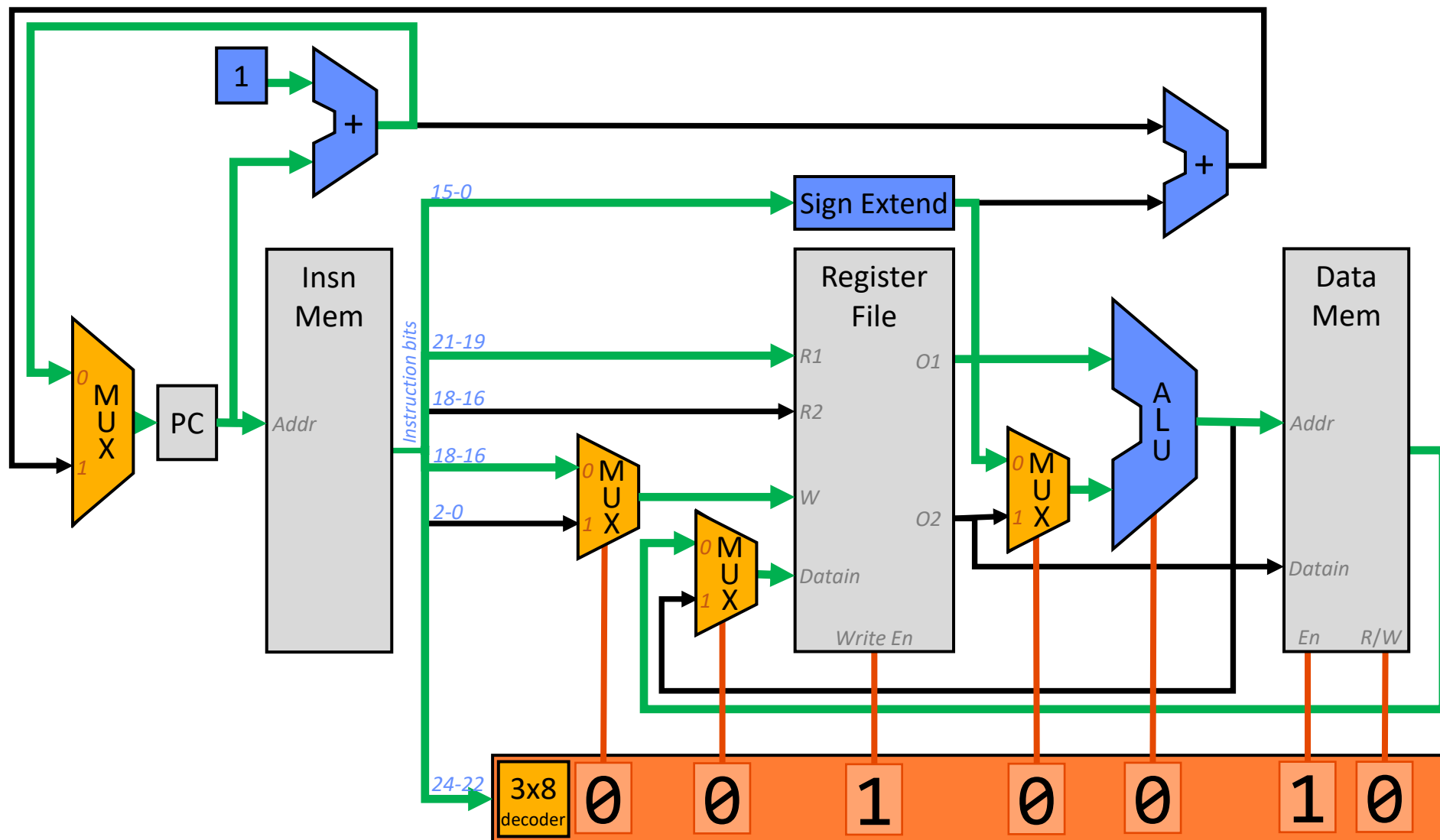

SW

Instruction	sw regA, regB, offset				
Functionality	$M[\text{regA} + \text{offset}] = \text{regB}; \text{PC} = \text{PC} + 1$				
I-Type	31-25	24-22	21-19	18-16	15-0
	opcode	regA	regB	destR	


LC2K Single-Cycle Processor

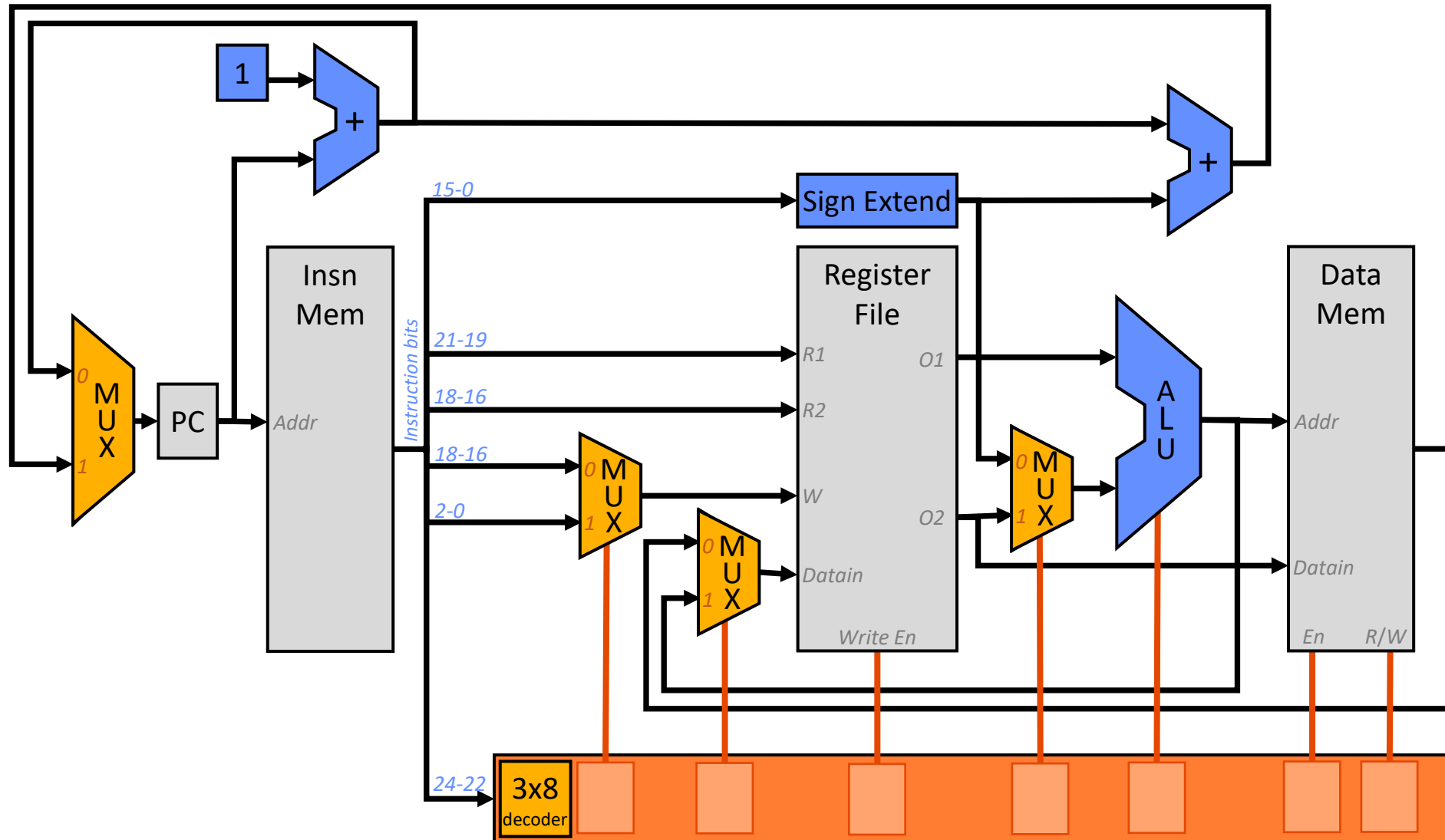

SW

Instruction	sw regA, regB, offset				
Functionality	$M[\text{regA} + \text{offset}] = \text{regB}; \text{PC} = \text{PC} + 1$				
I-Type	31-25	24-22	21-19	18-16	15-0
	opcode	regA	regB	destR	


LC2K Single-Cycle Processor

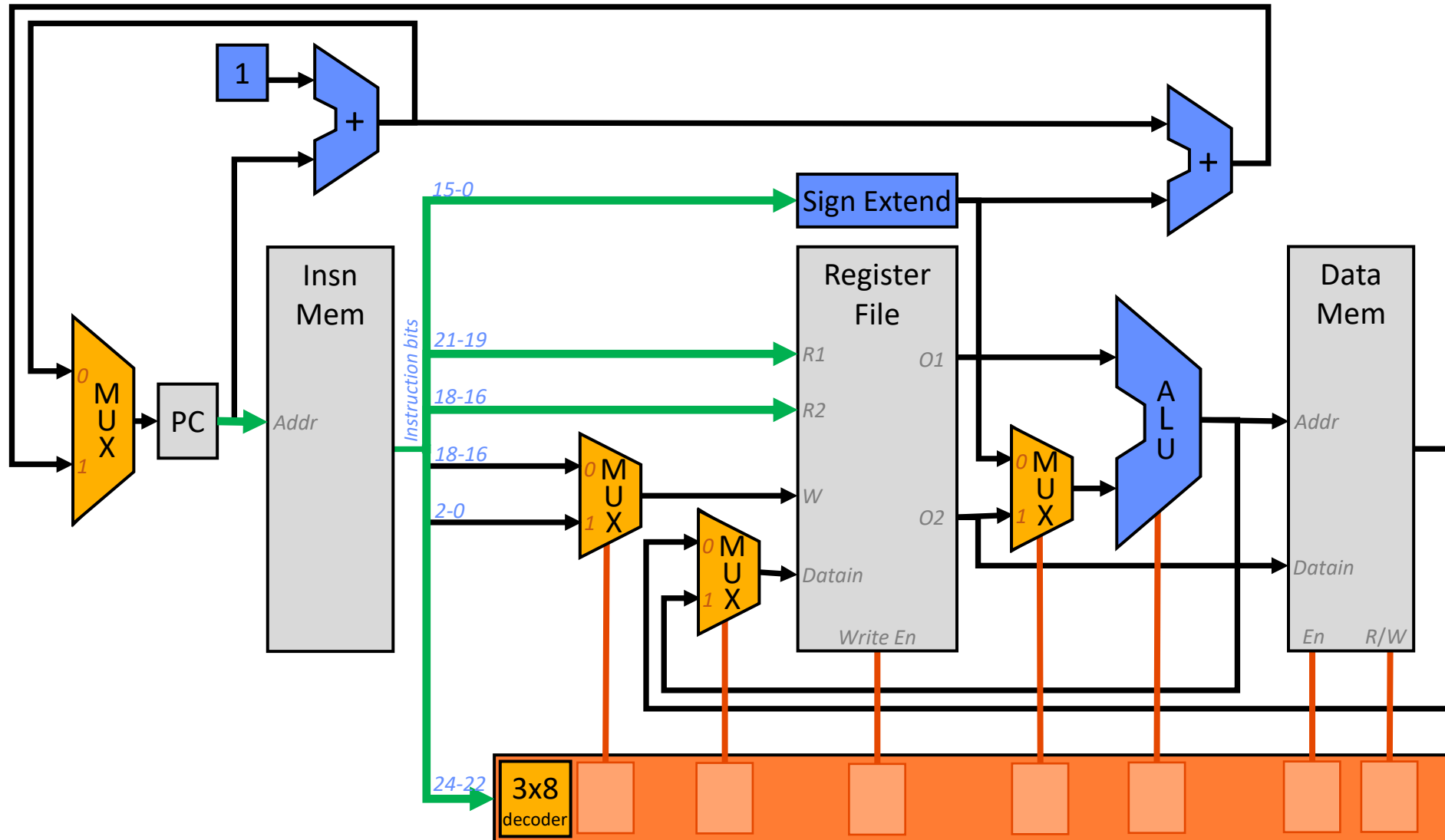

SW

Instruction	sw regA, regB, offset				
Functionality	$M[\text{regA} + \text{offset}] = \text{regB}; \text{PC} = \text{PC} + 1$				
I-Type	31-25	24-22	21-19	18-16	15-0
	opcode	regA	regB	destR	


LC2K Single-Cycle Processor

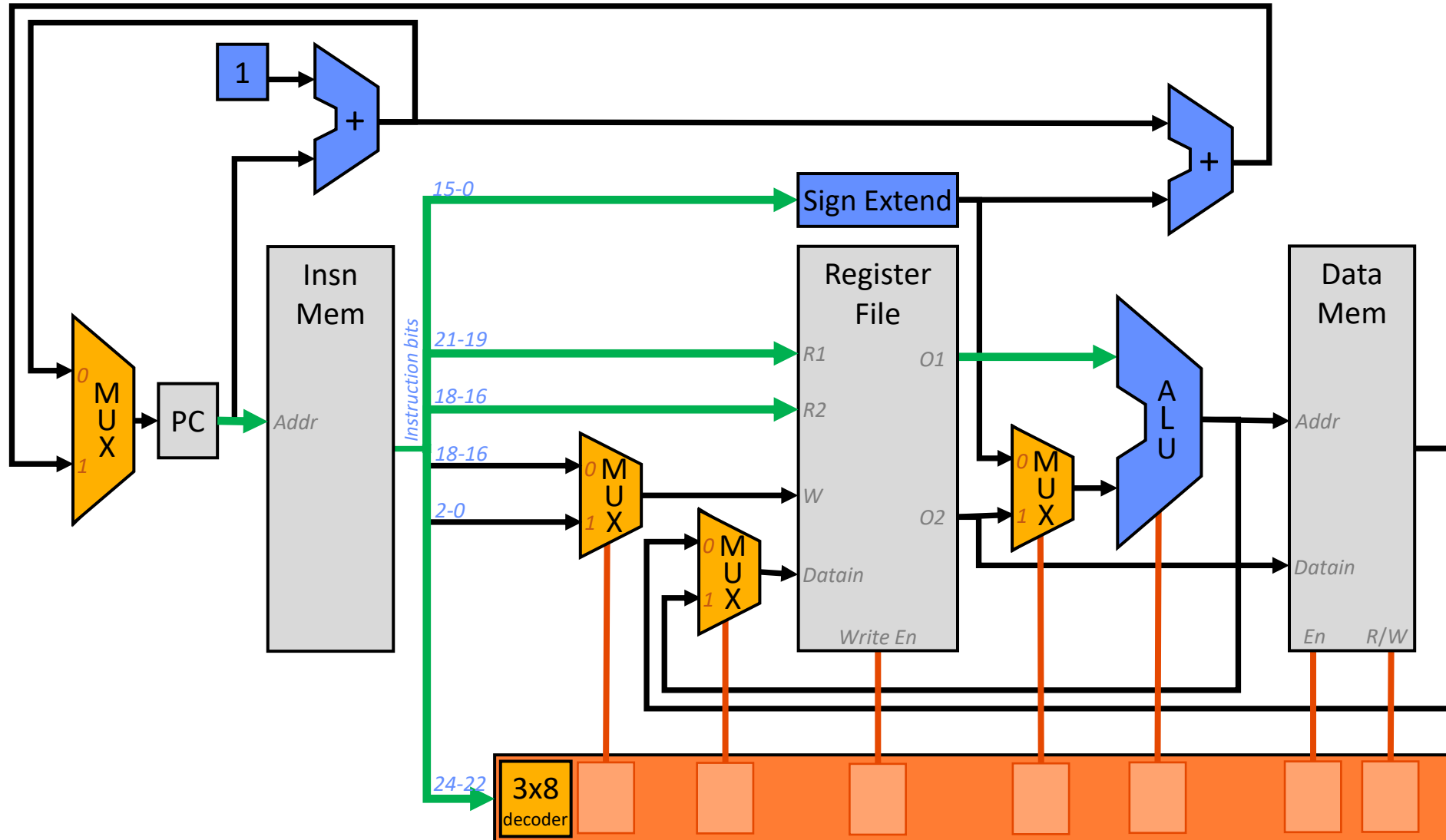

SW

Instruction	sw regA, regB, offset				
Functionality	$M[\text{regA} + \text{offset}] = \text{regB}; \text{PC} = \text{PC} + 1$				
I-Type	31-25	24-22	21-19	18-16	15-0
	opcode	regA	regB	destR	


LC2K Single-Cycle Processor

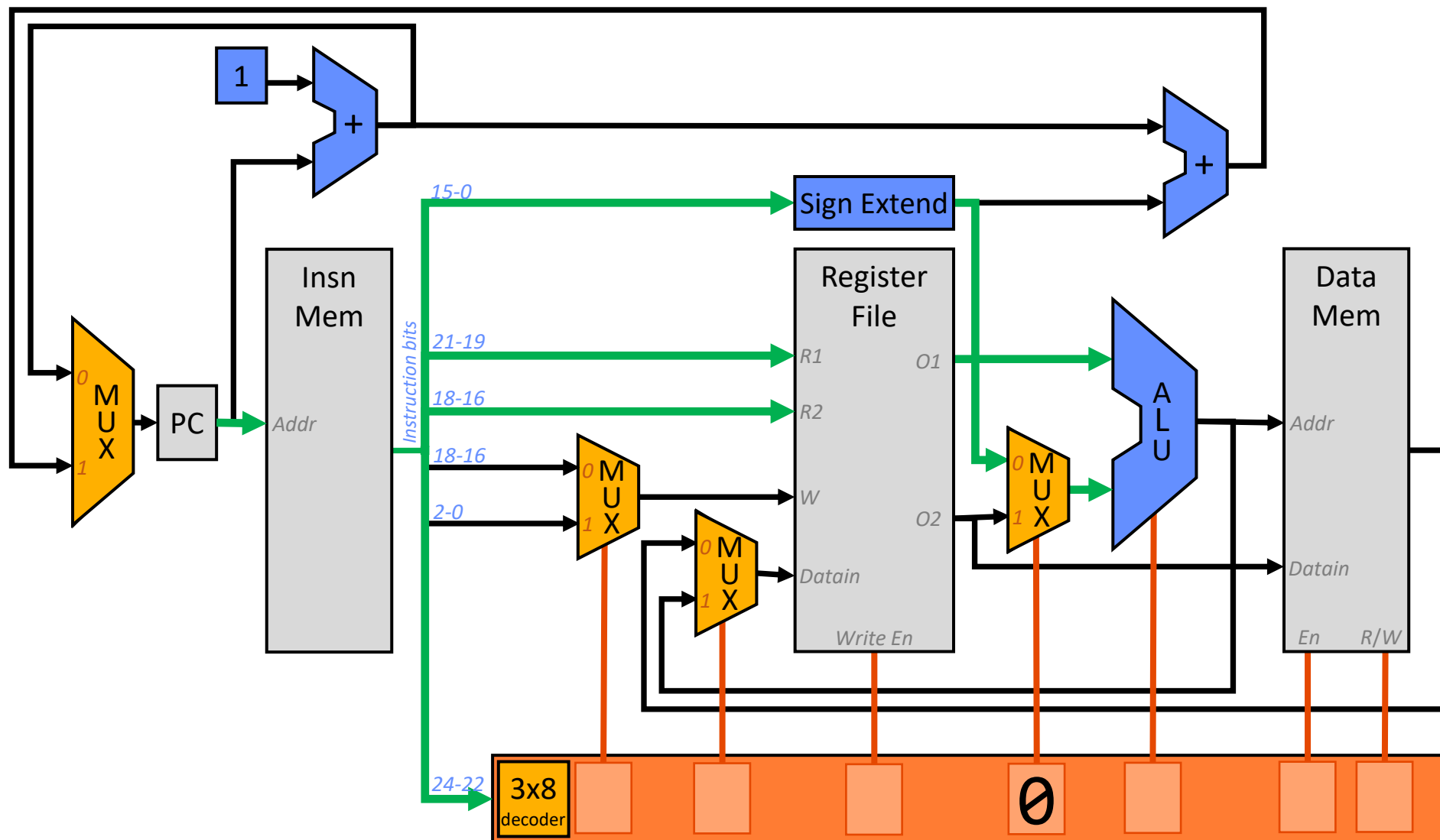

SW

Instruction	sw regA, regB, offset				
Functionality	$M[\text{regA} + \text{offset}] = \text{regB}; \text{PC} = \text{PC} + 1$				
I-Type	31-25	24-22	21-19	18-16	15-0
	opcode	regA	regB	destR	


LC2K Single-Cycle Processor

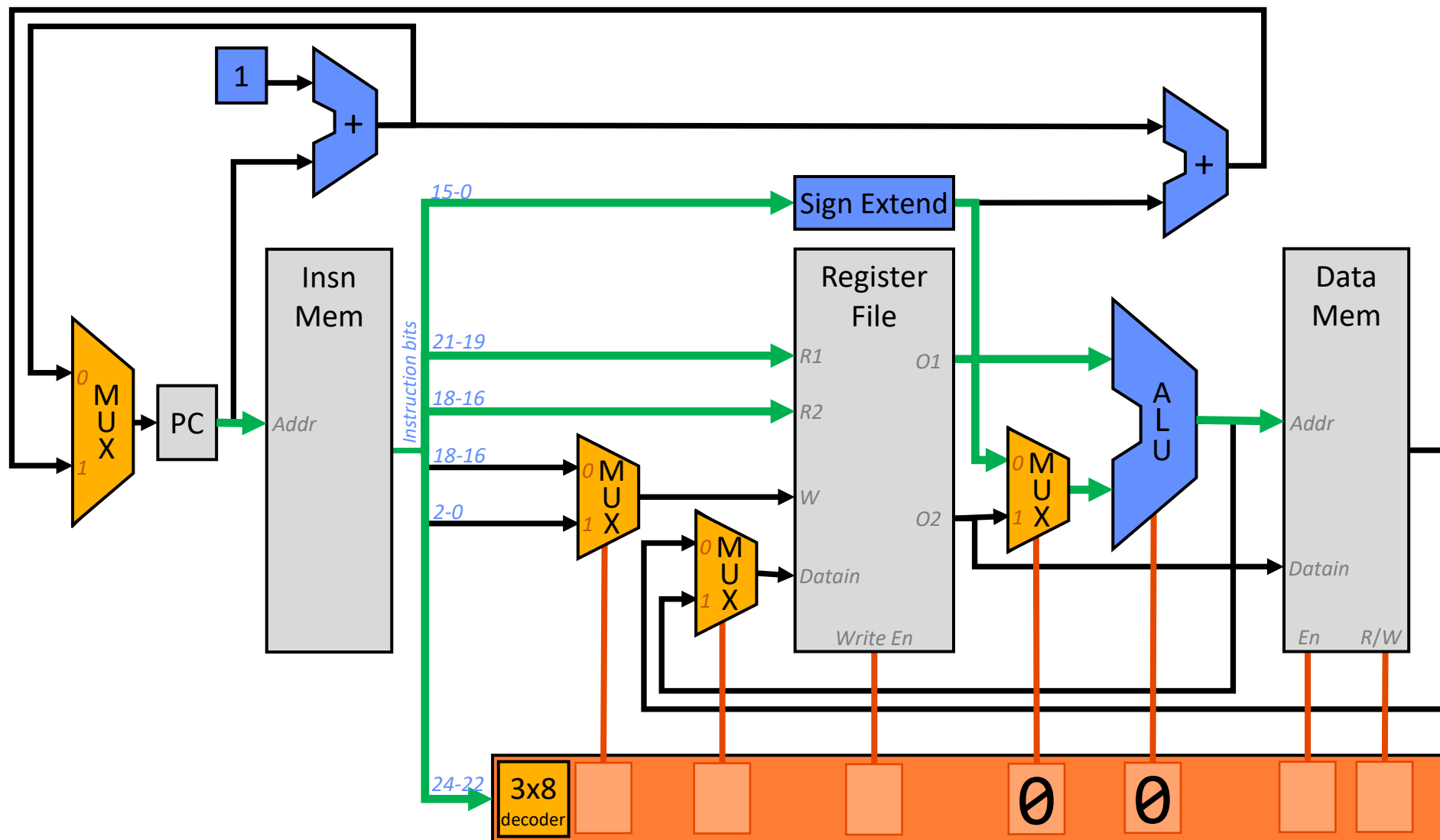

SW

Instruction	sw regA, regB, offset				
Functionality	$M[\text{regA} + \text{offset}] = \text{regB}; \text{PC} = \text{PC} + 1$				
I-Type	31-25	24-22	21-19	18-16	15-0
	opcode	regA	regB	destR	


LC2K Single-Cycle Processor

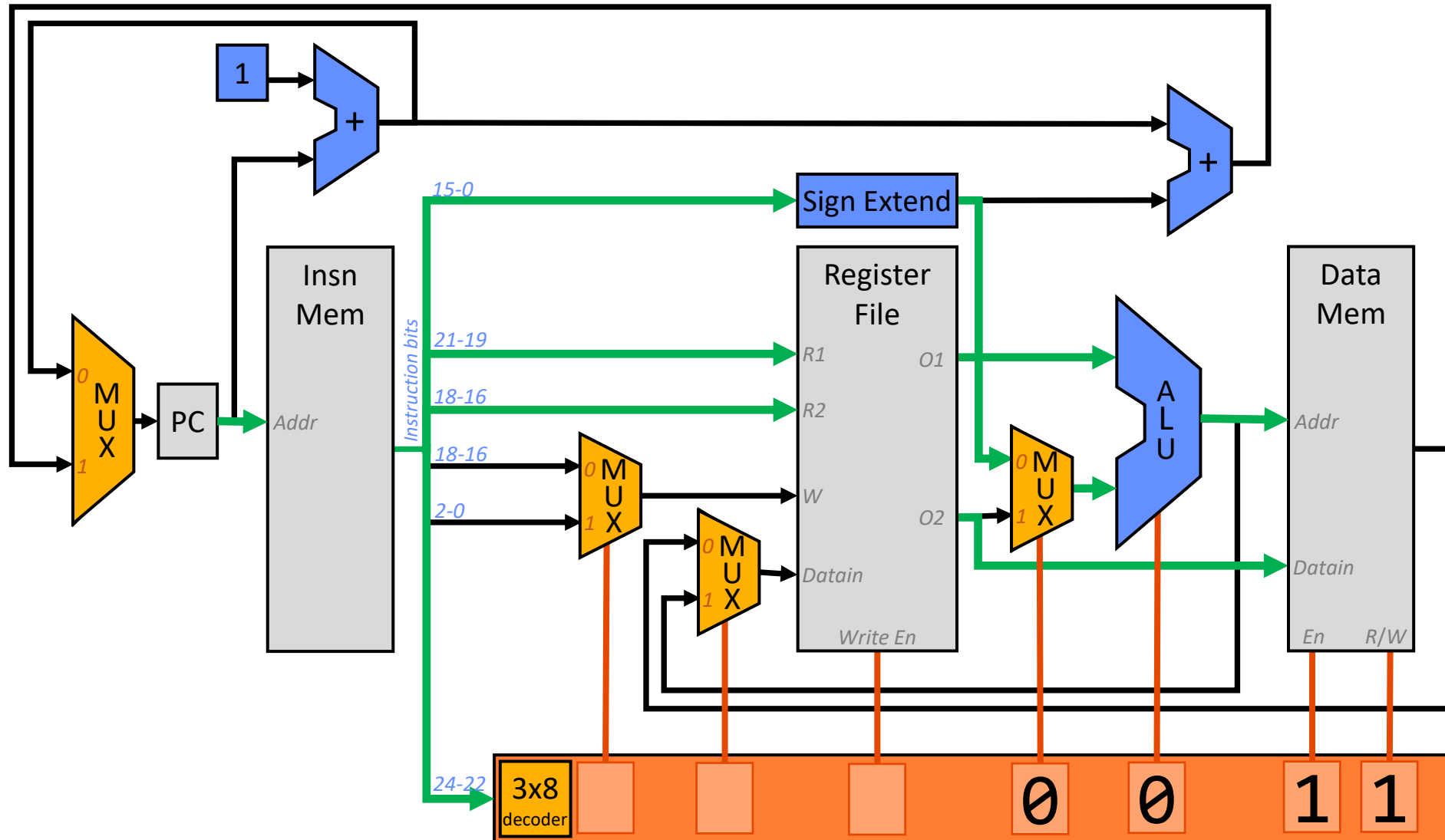

SW

Instruction	sw regA, regB, offset				
Functionality	$M[\text{regA} + \text{offset}] = \text{regB}; \text{PC} = \text{PC} + 1$				
I-Type	31-25	24-22	21-19	18-16	15-0
	opcode	regA	regB	destR	


LC2K Single-Cycle Processor

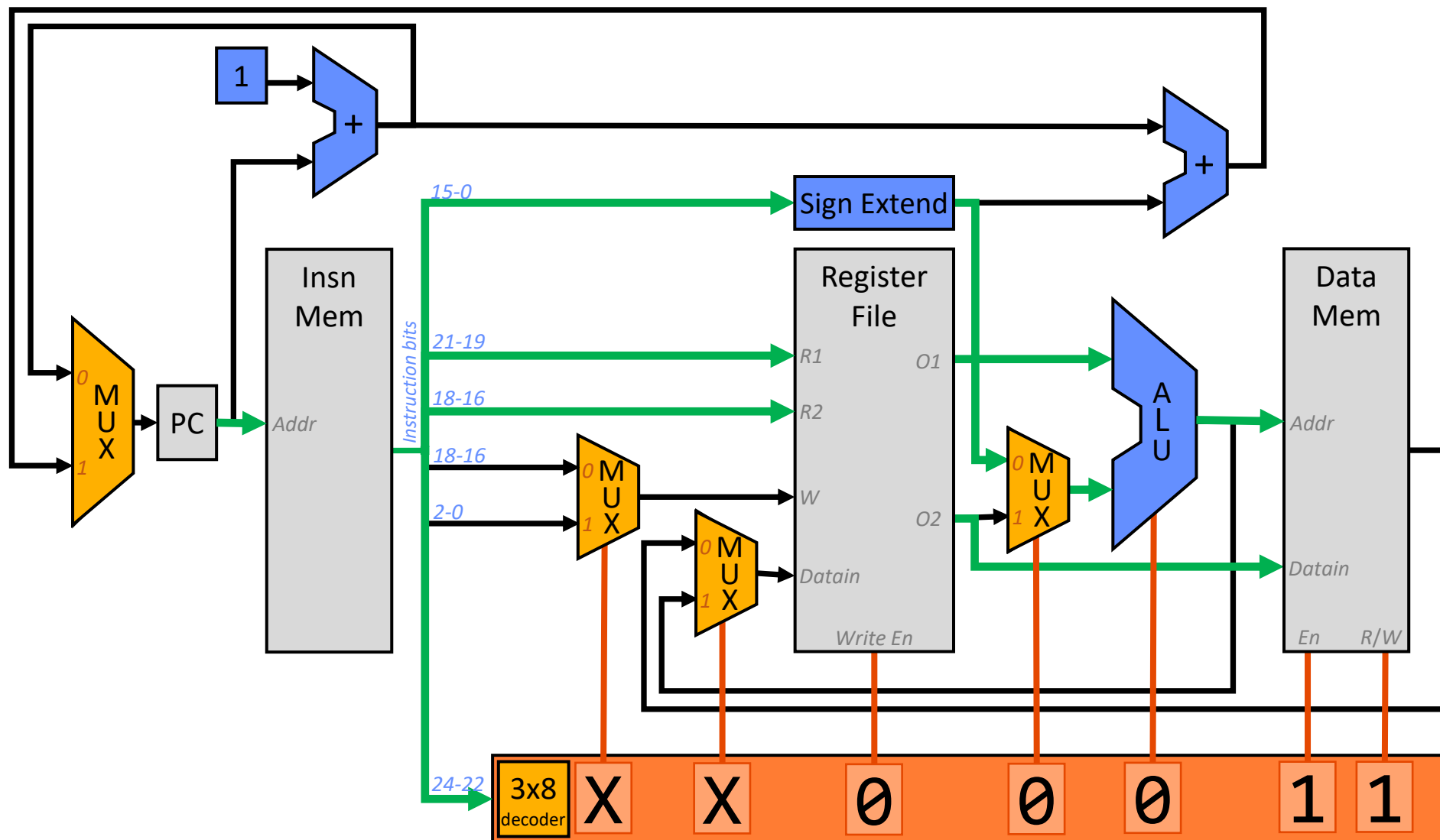

SW

Instruction	sw regA, regB, offset				
Functionality	$M[\text{regA} + \text{offset}] = \text{regB}; \text{PC} = \text{PC} + 1$				
I-Type	31-25	24-22	21-19	18-16	15-0
	opcode	regA	regB	destR	

LC2K Single-Cycle Processor

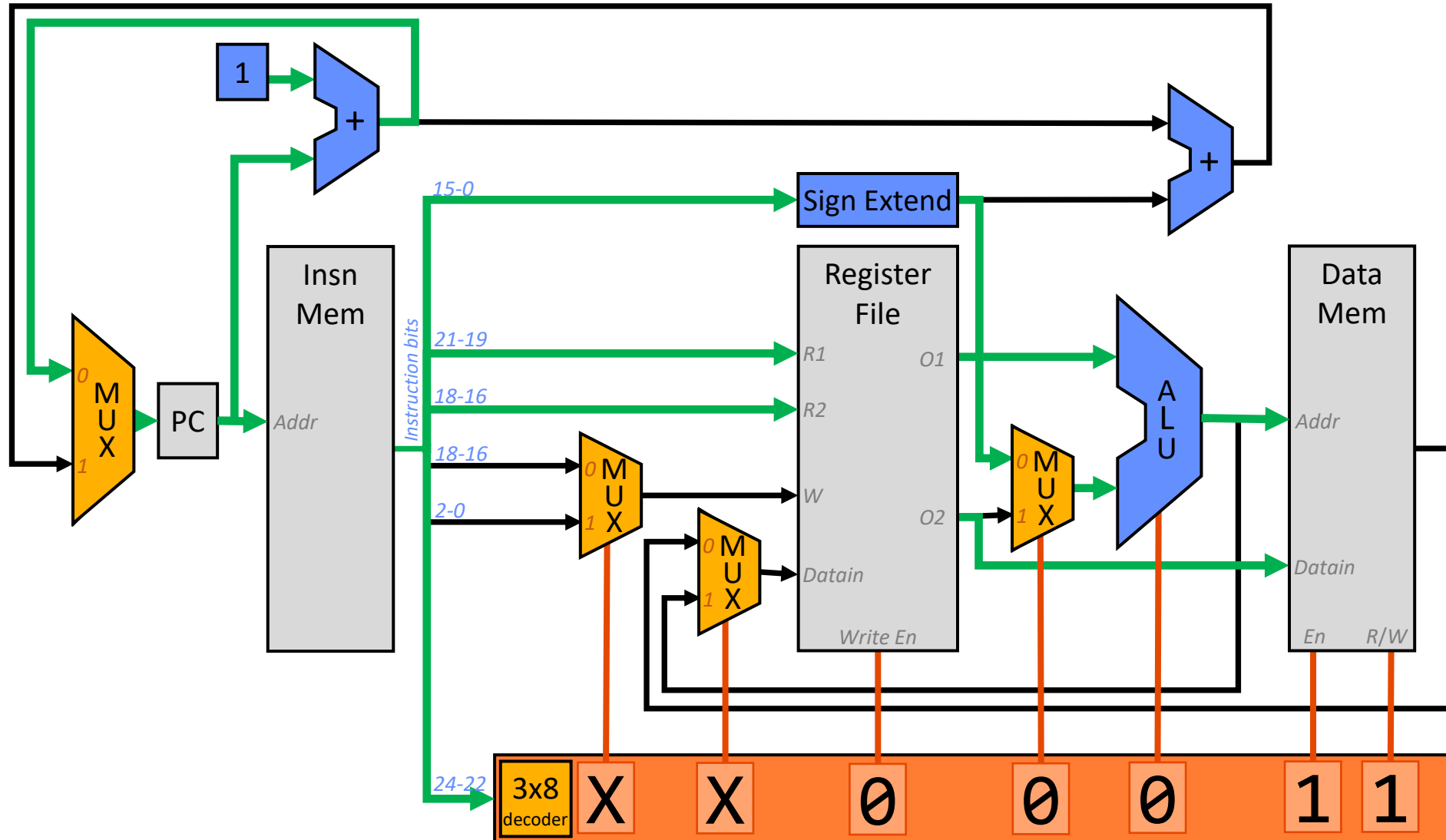



More instructions to come...

Next lecture!



Logistics

- There are 3 videos for lecture 10
 - L10_1 – Finite-State-Machines_Implementation
 - L10_2 – Single-Cycle-Processor
 - L10_3 – LC2K-Datapath
- There is one worksheet for lecture 10
 1. Finite state machine