



UM EECS 270 F21


Introduction to Logic Design

 3. Timing and Delay

Circuit Timing




- Logic circuits are physical structures built from electronic transistors and wires
- The digital abstraction *ignores physics* and assumes that circuits respond instantaneously
- In real implementations of logic circuits, we must account for *propagation delays*
 - Change at input of gate requires time to propagate through to output
 - Change at output of one gate requires time to reach input of next gate




- Digital circuits operate in distinctive steps:
 - 1) Apply inputs to circuit
 - 2) Wait for outputs to react
 - 3) Sample outputs at circuit

 - The speed of this process is determined by a **clock pulse** signal (often simply called a **clock**)



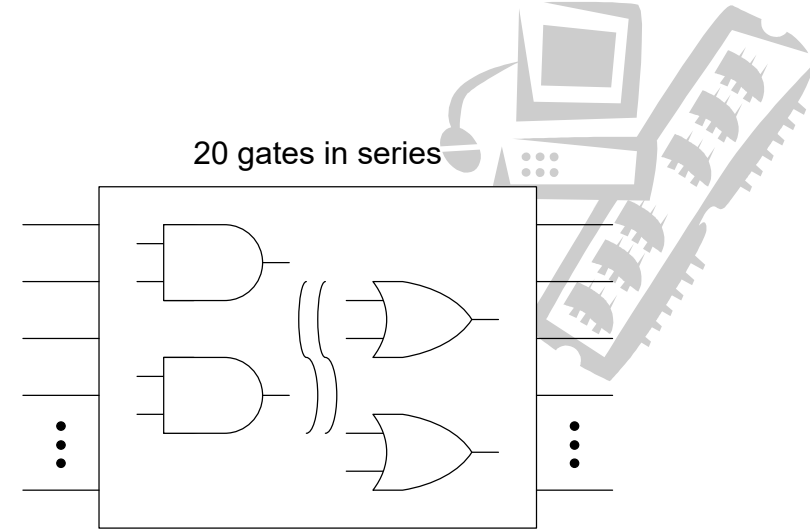- Circuits require a fixed time to respond to their inputs – it's important that circuits generate correct outputs *in the allotted time*
 - Being late is as bad as being wrong!



How fast can this circuit be “clocked” if each gate has a delay of 5ns?

$$20 * 5\text{ns} = 100\text{ns}$$



$$1 / 100\text{ns} = \mathbf{10\text{MHz}}$$

What if each gate has a delay of 50ps?

$$20 * 50\text{ps} = 1\text{ns}$$

$$1 / 1\text{ns} = \mathbf{1\text{GHz}}$$

Timing Diagrams

 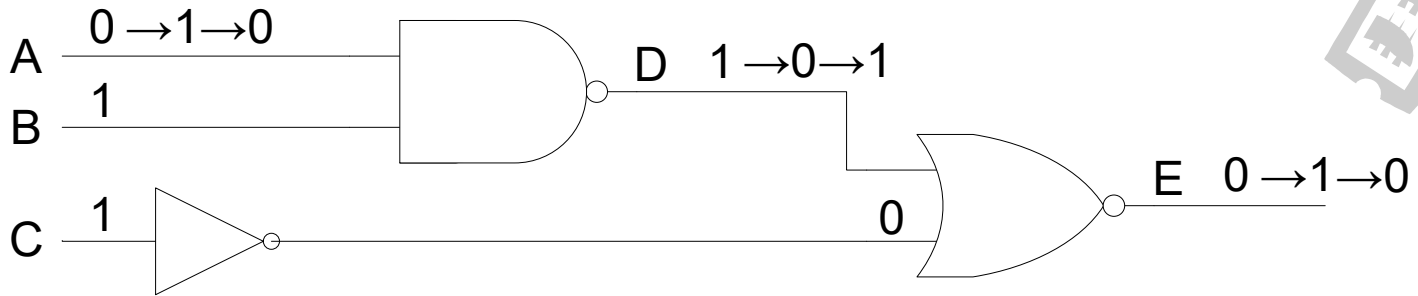

Causality Arrow



Gate Propagation Delay


$$t_{pHL}^{NAND}$$

gives NAND gate propagation delay from input to output when output is changing from H to L




- In general, for a particular gate, $t_{pHL} \neq t_{pLH}$
- Gate delays vary with operating conditions:
 - Operating voltage
 - Temperature
 - Output capacitance
- Therefore, IC designers typically specify:
 - Minimum delay: best case (not very useful!)
 - Maximum delay: worst case
 - Typical delay: “normal” operating conditions
- Often, we’ll use $t_p = \max(t_{pHL}, t_{pLH})$ for simplicity

Propagation delay in nanoseconds of 74LS family

Part Number	Typical		Maximum	
	t_{pLH}	t_{pHL}	t_{pLH}	t_{pHL}
00, 01	9	10	15	15
02	10	10	15	15
04	9	10	15	15
08, 11	8	10	15	20
14	15	15	22	22
20	9	10	15	15
21	8	10	15	20
27	10	10	15	15
30	8	13	15	20
32	14	14	22	22
86	12	10	23	17

 

Multiple paths from input to output

 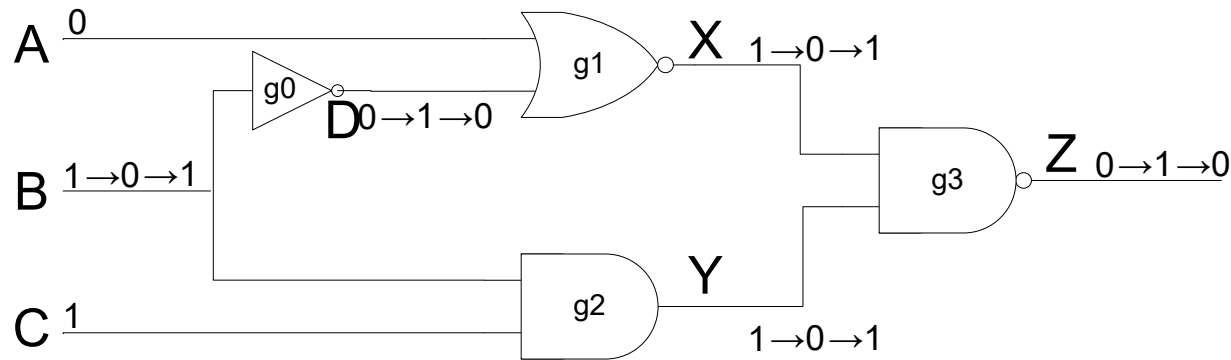 

Assume all rising and falling gate delays are 1ns:


$$t_{pLH}^{B \rightarrow Z} = t_{pHL}^{g2} + t_{pLH}^{g3} = 2ns$$

$$t_{pHL}^{B \rightarrow Z} = t_{pHL}^{g0} + t_{pLH}^{g1} + t_{pHL}^{g3} = 3ns$$

The overall circuit delay depends on the transition path taken from the inputs to the output




Unit-Delay Timing Simulation

 



A “Slightly” More Realistic Delay Model



Delay \propto Transistor Resistance

 

A “Slightly” More Realistic Delay Model

  

#(2,1)

$$\#(\frac{2 \times 2}{2 + 2}, 1 + 1) \\ = \#(1, 2)$$


$$\#(2 + 2, \frac{1 \times 1}{1 + 1}) \\ = \#(4, 0.5)$$

$$\#(2 + 2, 1 + 1) \\ = \#(4, 2)$$




Rise/Fall-Delay Timing Simulation


Bi-Stable Circuit & Ring Oscillator

 

This circuit is **bi-stable**

 

 This circuit is known as a **ring-oscillator**



$$t_{period} = t_{pHL}^{g1} + t_{pLH}^{g2} + t_{pHL}^{g3} + t_{pLH}^{g1} + t_{pHL}^{g2} + t_{pLH}^{g3}$$

Assume all gate delays are 1ns:

$$t_{period} = 6ns \quad f_{osc} = \frac{1}{6ns} = 166MHz$$